
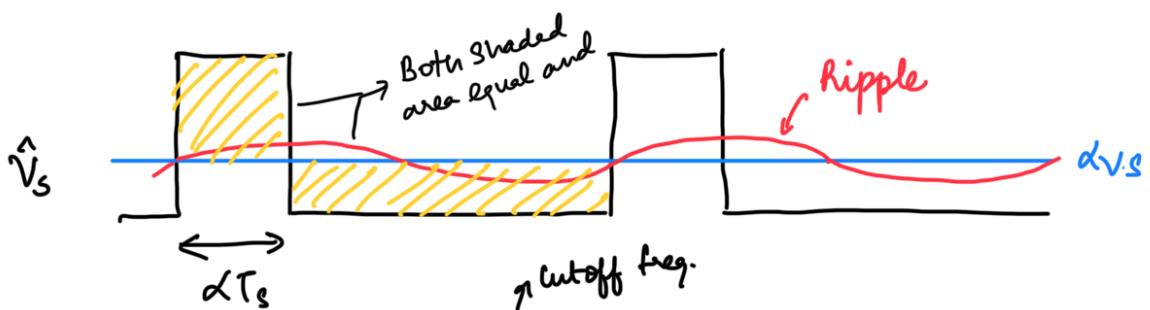


DC-DC Converters

Lossless ways of converting DC Voltages

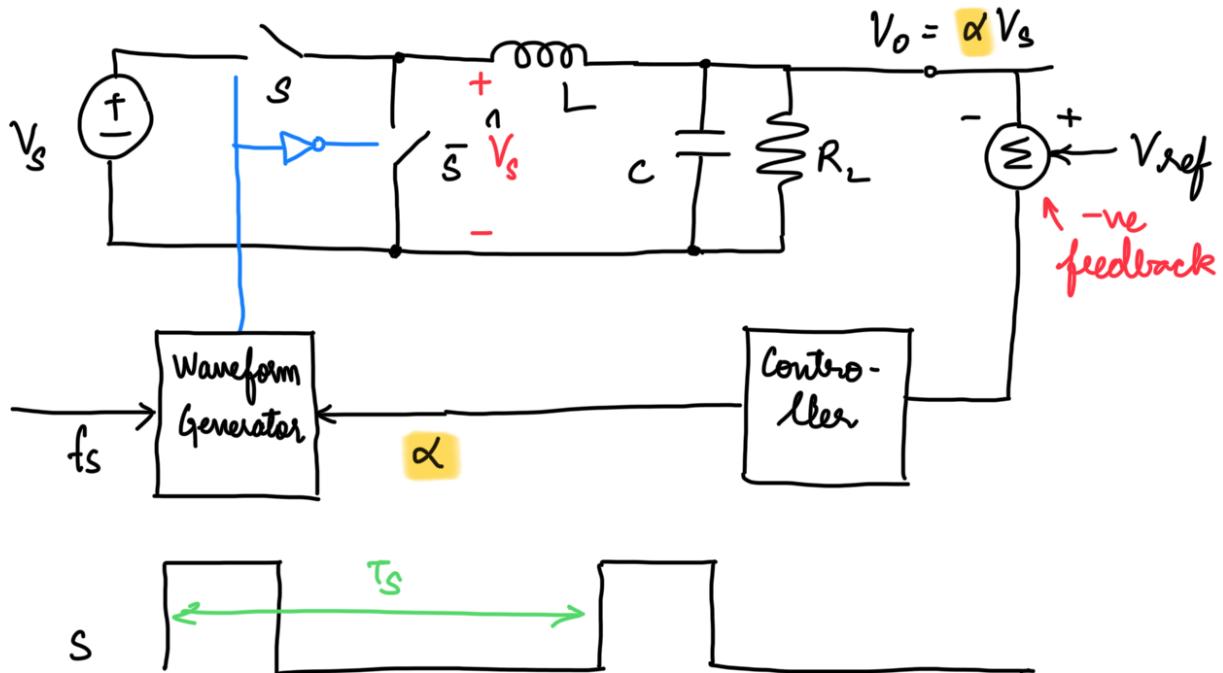We already have seen a topology to obtain average voltages lower than source voltage using **switches** and **low pass filters (lossless LC)**




$$f_S \geq \frac{1}{2\pi\sqrt{LC}} \rightarrow \text{Ripple Amplitude drops and we get Nearly DC voltage!}$$

Now, since we have a negative feedback loop, we need to make sure it is stable.

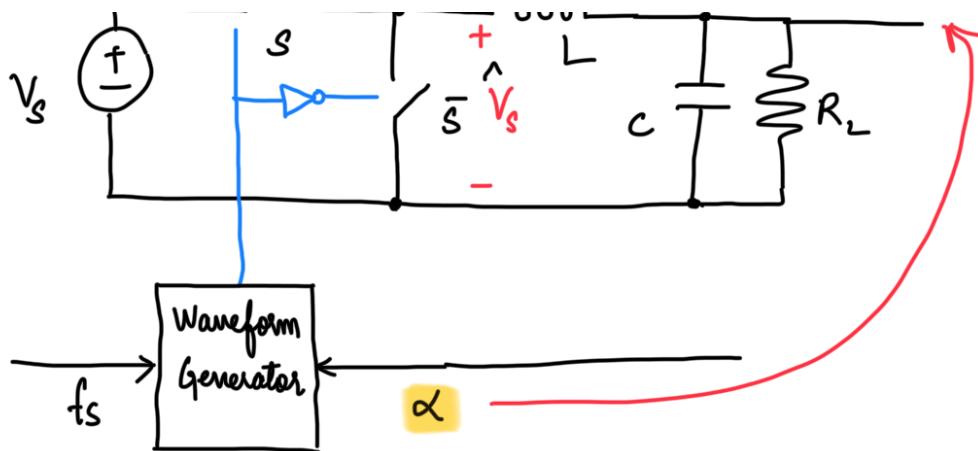And for that, we need the loop gain - And for that we need the model of this circuit.






Transfer function - ? \rightarrow we'll need impulse response.

How to determine the impulse response? \rightarrow

\int We'll try to evaluate the step response.

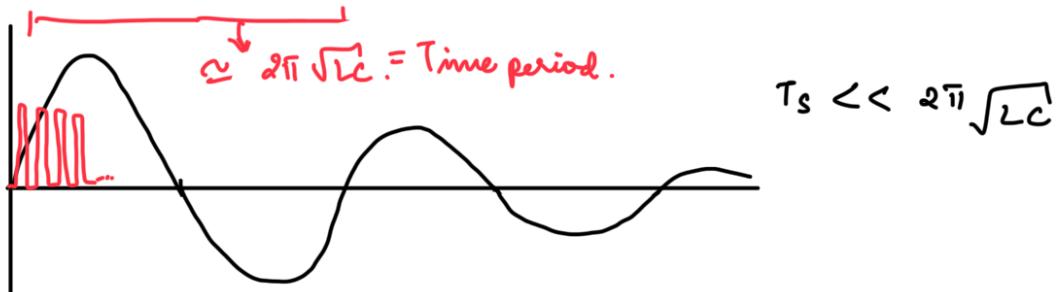For ease of calculation, let α : in the beginning.



We now are basically convolving the α [which is now the input voltage] and the system's $x(t) \rightarrow$ RLC circuit!

$$\therefore \int h(\tau) x(t-\tau) d\tau = h_0 \int x(t-\tau) d\tau .$$


Impulse response of the LC filter hardly changes within a switching period.
 \uparrow Approximation!

- * The input can be approximately represented by its average in each period.

Response of the circuit to a step d_0 in the duty cycle
 \simeq Response of the LTI (LPF) to a step $d_0 V_s$

Now: The transfer function: What is it?

$$\frac{V_o(s)}{\alpha(s)} = ?$$

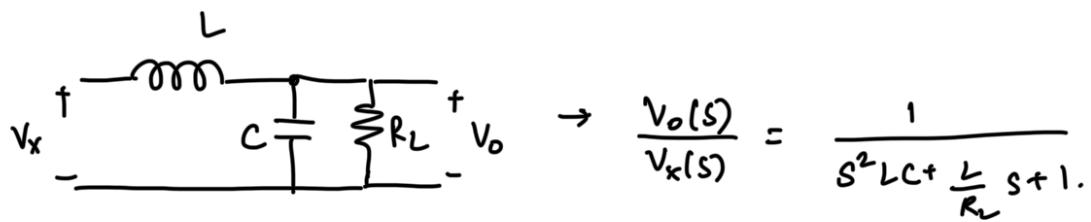


But $V_x(s) = \alpha(s) V_s$.


$$\therefore \frac{V_o(s)}{\alpha(s)} = V_s \cdot \frac{1}{s^2 LC + s \frac{L}{R_L} + 1}$$

Now that we have the transfer function, we will now look at the loop gain, find the phase margin, and study the stability of the negative feedback that we encountered..

α cannot vary rapidly ... NOTE.

Let's bode plot $V_o(s)/\alpha(s)$.

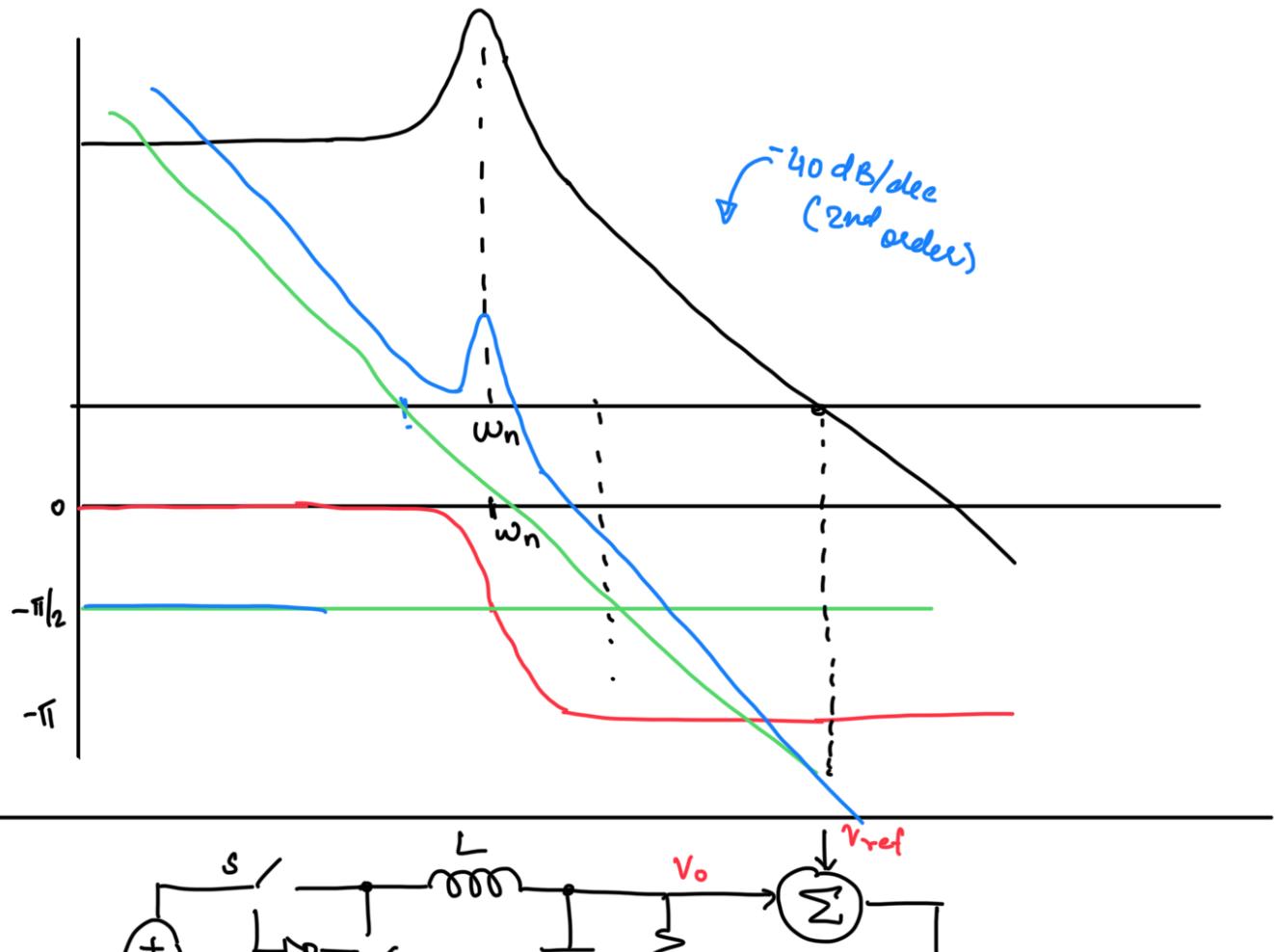

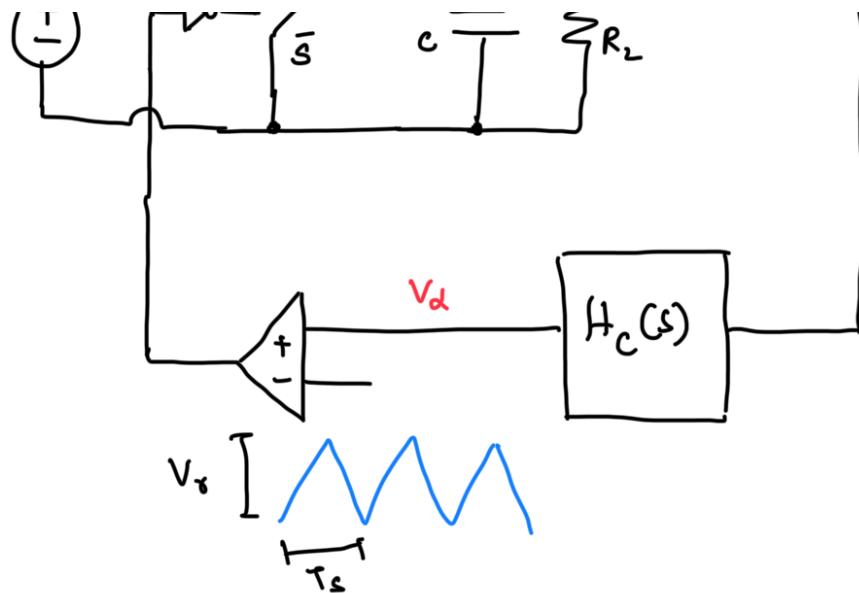

$$H_c \frac{V_o}{V_d} = \text{Loop Gain} \rightarrow \text{Must have appropriate phase margin}$$


We want H_c to have high gain in DC. $\omega_c / s_+ = H_c$ [for now].

Basically an integrator: $H_c = \frac{\omega_c}{s}$. What/ How should ω_c be?

@ $\frac{1}{\sqrt{LC}}$: $\frac{V_s}{V_d}$ has its peak ; Peak = $\frac{V_s}{V_r} \Omega$.

$$H_c \left(j \frac{1}{\sqrt{LC}} \right) < \frac{1}{\frac{V_s}{V_r} \Omega} ; \quad \omega_c < \frac{\omega_n}{\frac{V_s}{V_r} \cdot \Omega}$$

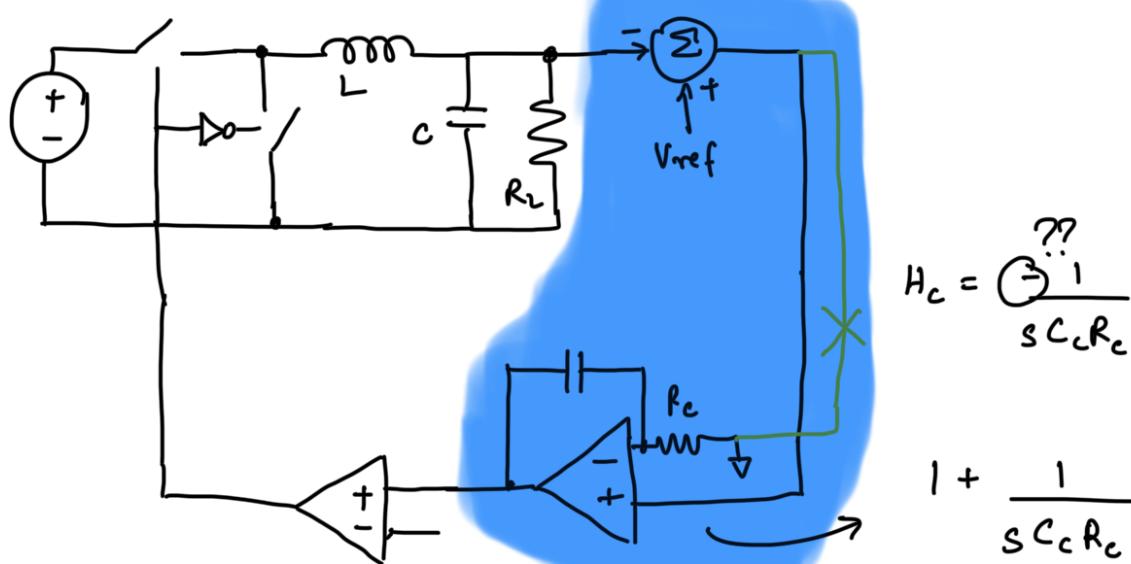Now that we've figured out that H_c must be an integrator :




$$W_{uf} = \omega_c \cdot \frac{V_s}{V_r} = \frac{1}{C_c R_c} \cdot \frac{V_s}{V_r}$$

$C L B = W_{uf}$ if the system is ideal -

We will now try to implement this part of the circuit...


For addition - summing amplifier?

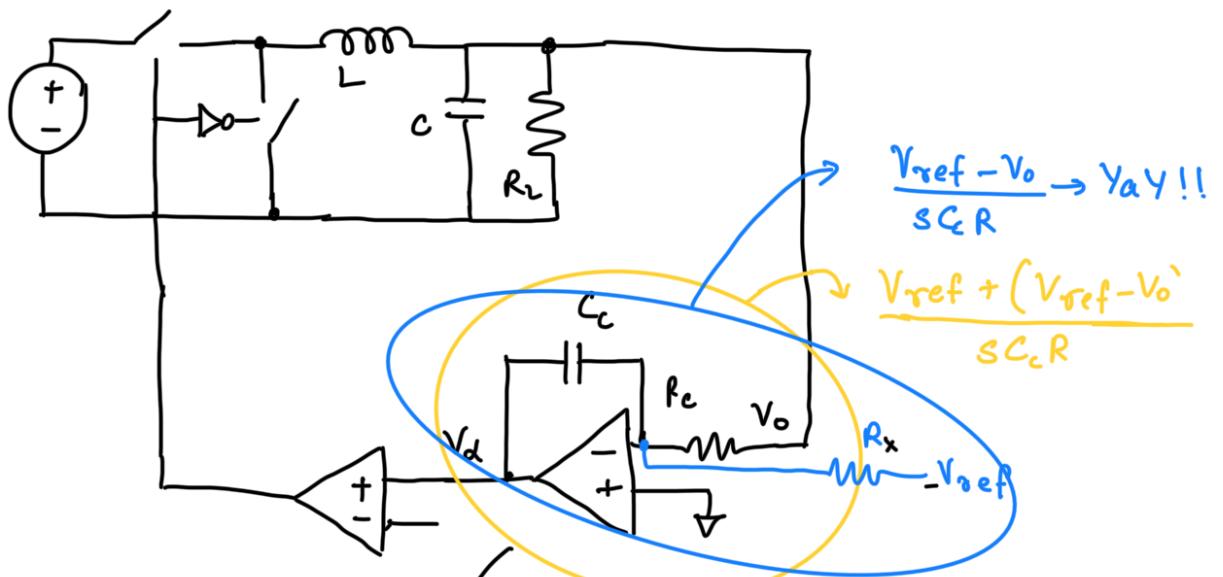

We now have a summing integrator, instead of a summing amplifier.


But we usually compare an attenuated version of V_o with V_{ref} .

∴ The modified circuit is now:

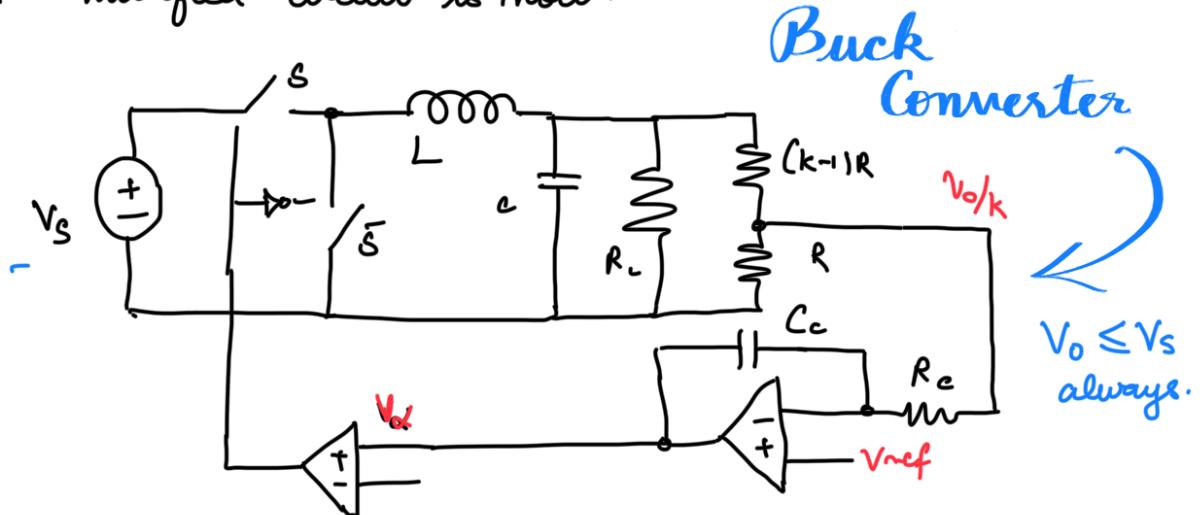

Waveform across inductor...

$$D_L = \int \frac{V_L}{V_s} dt$$

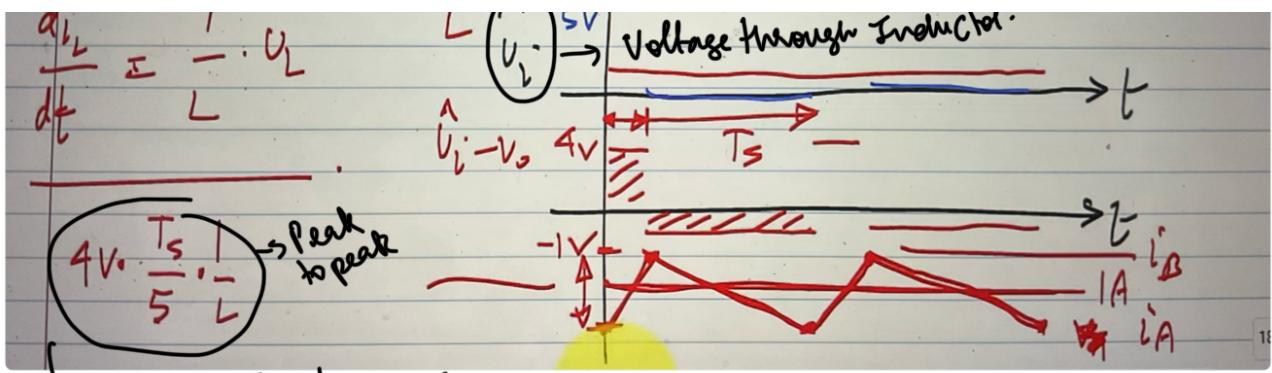


This is taking $V_s = 5V$, $\alpha = \frac{1}{5}$.

Now after the inductor, the ripple goes through the capacitor and the DC part will go through the resistor \Rightarrow Which is exactly what we want.

If this is the current flowing through the inductor, if R is high, then it flows into the capacitor.

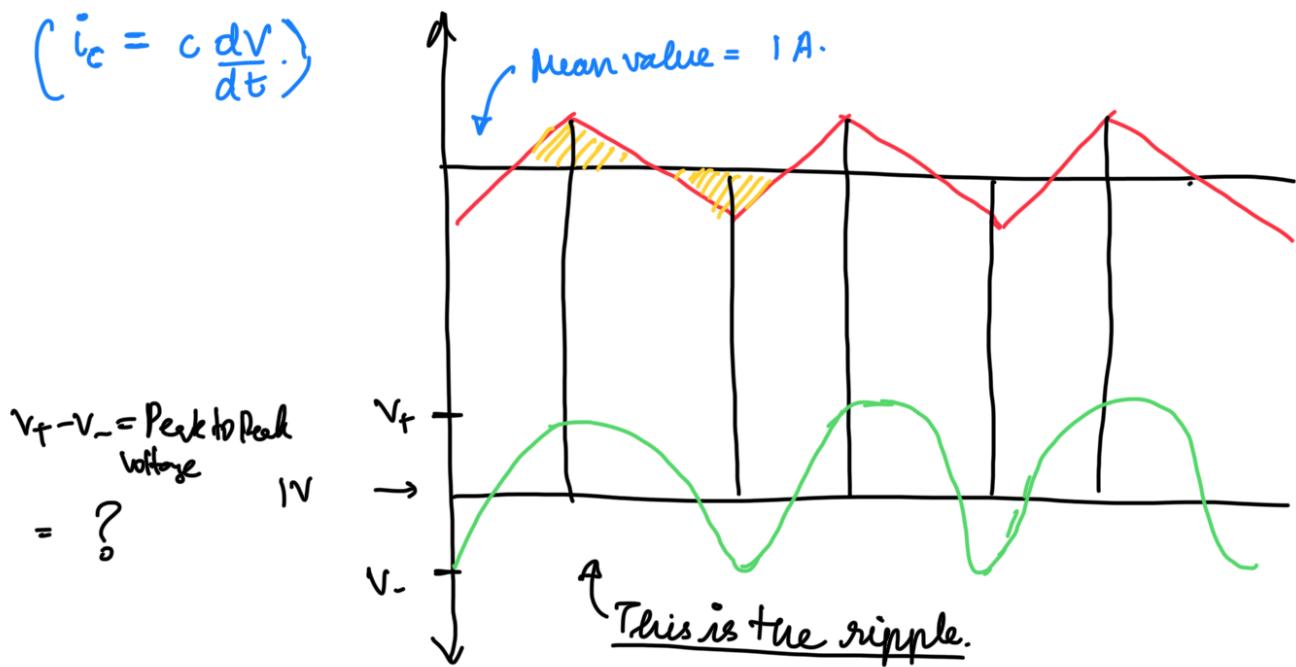So, what would be the capacitor voltage? - Parabolae?




and we need the peak-peak voltage to be as less as possible !! ?!

We'll look at how to get $\propto v_i$ from v_i .




→ Trivial right? — Non-inverting amplifier.

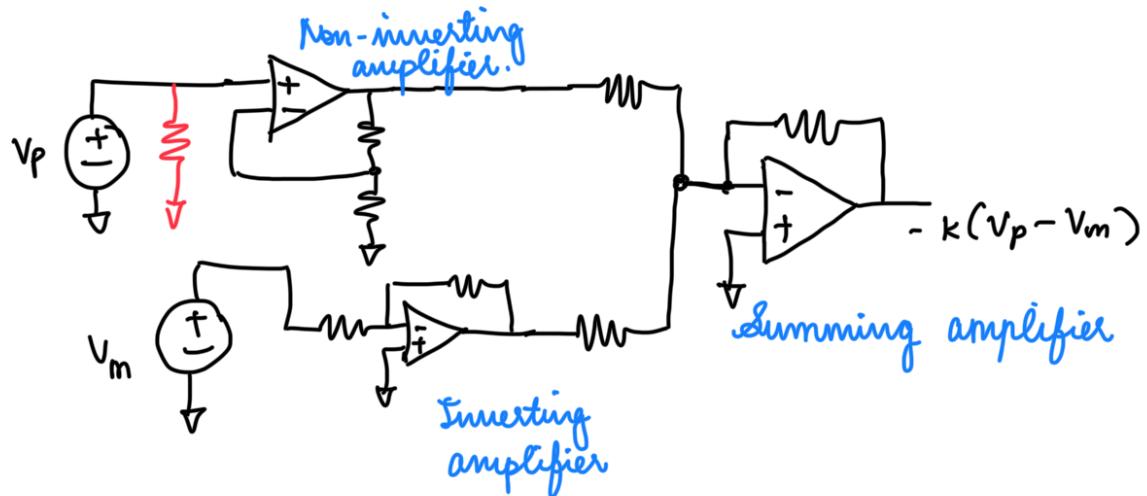But what about getting $k(V_p - V_m)$ from V_p & V_m ?



Is there a way to do all of this with lesser OpAmp? Yes!

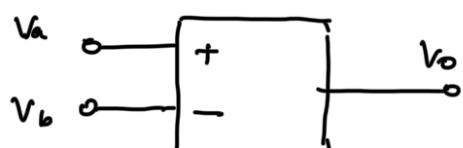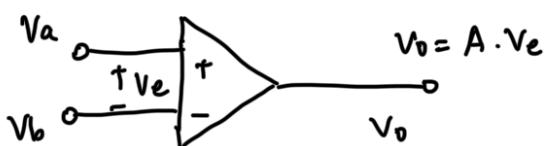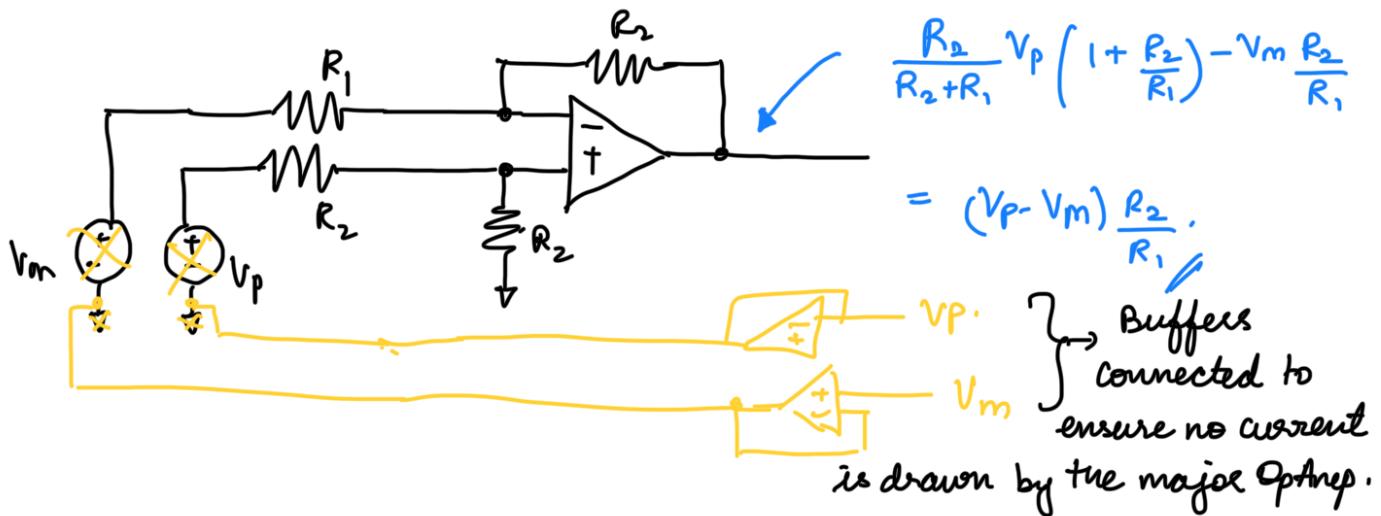Infact, we can do it with just one OpAmp!! How? :



$$V_o = \alpha V_a + \beta V_b$$

For an opAmp, $\alpha = -\beta$.

[For any general 3-terminal device]

$$V_d = (V_a - V_b)$$

$$V_{cm} = \frac{V_a + V_b}{2}$$

Common mode voltage

(differential component)

$$V_{cm} = \frac{V_a + V_b}{2} \quad (\text{average}).$$

$$V_a = V_{cm} + V_d/2 \quad ; \quad V_b = V_{cm} - V_d/2.$$


Ideally, $\alpha = -\beta$ for opAmp. But it is never perfect.

$$V_o = \alpha V_a + \beta V_b = \frac{\alpha - \beta}{2} V_d + \frac{\alpha + \beta}{2} V_{cm}.$$

$$= A_d V_d + A_{cm} V_{cm}$$

differential gain. common mode gain

Difference Amplifier:

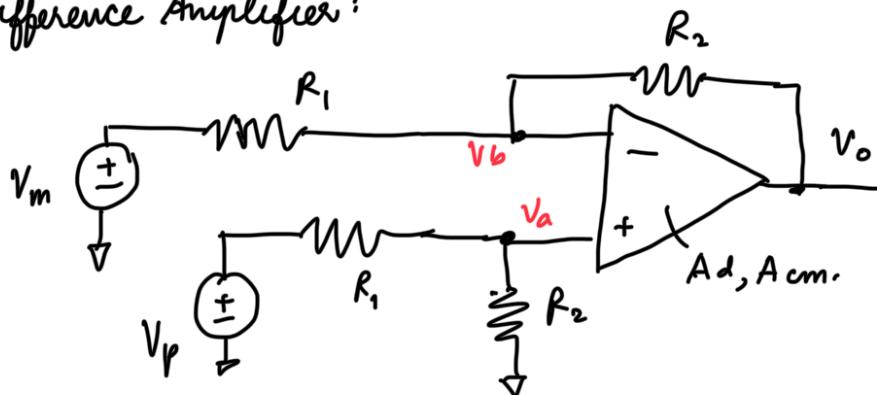

$$V_a = V_m \frac{R_2}{R_2 + R_1} \quad ; \quad V_b = \frac{V_o R_1}{R_1 + R_2}.$$

$$V_o = A_d \cdot V_d + A_{cm} \cdot V_{cm}.$$

$$V_d = \frac{(V_p - V_m) R_2}{R_1 + R_2} - \frac{V_o R_1}{R_1 + R_2}; \quad V_{cm} = \frac{V_p + V_m}{2} \frac{R_2}{R_1 + R_2} + \frac{V_o R_1}{2(R_1 + R_2)}.$$

$$= A_d (V_p - V_m) \left[\frac{R_2}{R_1 + R_2} \right] - A_d V_o \cdot \frac{R_1}{R_1 + R_2}$$

$$+ A_{cm} \left(\frac{V_p + V_m}{2} \right) \frac{R_2}{R_1 + R_2} + \frac{A_{cm}}{2} \left(\frac{V_o R_1}{R_1 + R_2} \right)$$


$$\therefore V_o = \left(A_d (V_p - V_m) \frac{R_2}{R_1 + R_2} + A_{cm} \left(\frac{V_p + V_m}{2} \right) \frac{R_2}{R_1 + R_2} \right)$$

$$\begin{aligned}
 & \left(\frac{\left(1 + Ad - \frac{A_{cm}}{2} \right) \cdot \frac{R_1}{R_1 + R_2}}{\left(1 - \frac{A_{cm}}{2Ad} + \frac{1}{Ad} \left(\frac{R_1 + R_2}{R_1} \right) \right)} \right) \div Ad \frac{R_1}{R_1 + R_2} \\
 = & (V_p - V_m) \frac{R_2}{R_1} \cdot \frac{1}{1 - \frac{A_{cm}}{2Ad} + \frac{1}{Ad} \left(\frac{R_1 + R_2}{R_1} \right)} \\
 & + \left(\frac{V_p + V_m}{2} \right) \cdot \frac{R_2}{R_1} \cdot \frac{\overbrace{A_{cm}/Ad}^{\text{Not good...}}}{1 - \frac{A_{cm}}{2Ad} + \frac{1}{Ad} \left(\frac{R_1 + R_2}{R_1} \right)}
 \end{aligned}$$

Ad/A_{cm} → Called as the Common mode Rejection Ratio.

Instrumentation Amplifier

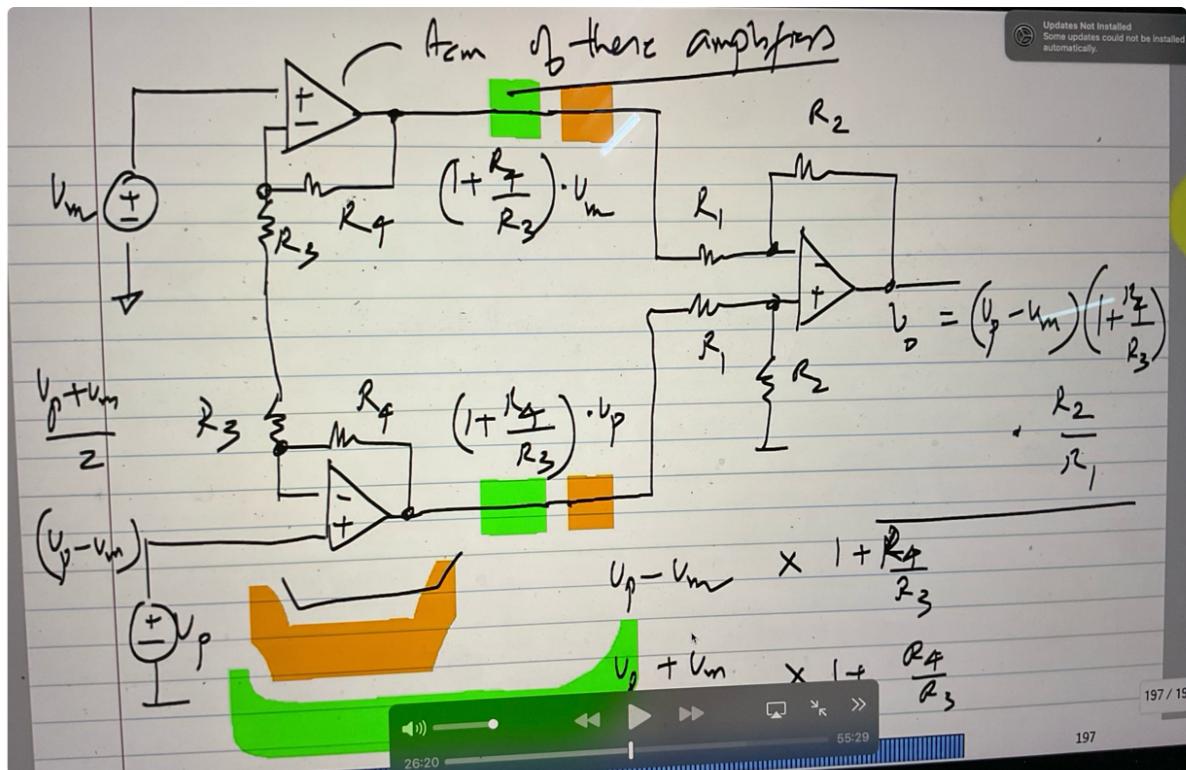Something similar to CMRR → PSRR (Power supply rejection Ratio)



What is the difference between the previous circuit and the current circuit?

$$V_o = (V_p - V_m) \left(1 + \frac{R_4}{R_3} \right) \cdot \frac{R_2}{R_1} \cdot \frac{1}{1 + \frac{R_4}{R_3}} + \left(\frac{V_p + V_m}{2} \right) \left(1 + \frac{R_4}{R_3} \right) \cdot \frac{R_2}{R_1} \cdot \frac{A_{cm}}{1 + \frac{R_4}{R_3}}$$

3 opamp instrumentation Amplifier.

