

6 Nagendra Krishnapura Analog Notes

Filters

Frequency selective circuits

How to make filters $\rightarrow R_s, L_s + C_s$. Mostly C_s as L_s are bulky.

But we'll try implementing filters using active elements (semiconductor devices). \rightarrow Active filters.

Filters have a vital application in Sampling.



Synthesising first and second order filters

- \rightarrow Channel selection
- \rightarrow Noise removal
- \rightarrow Anti-aliasing
- \rightarrow Reconstruction

Filter:

$$H(s) = \frac{N(s)}{D(s)} = \frac{V_o}{V_i}$$

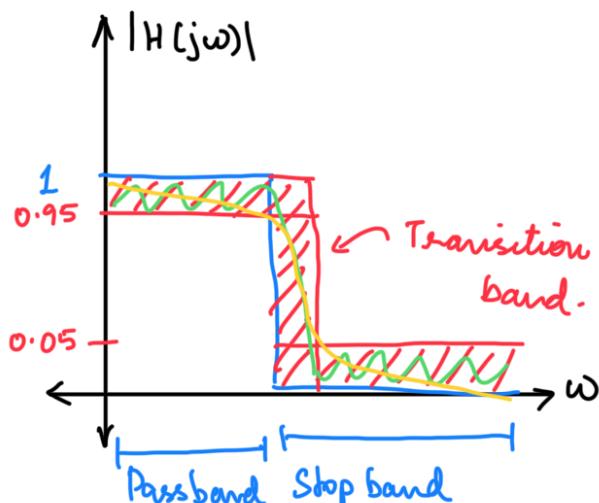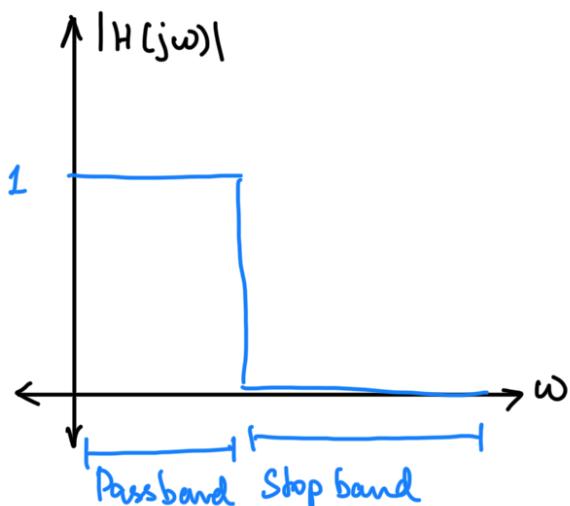Filter synthesis - obtain $N \times D$ from specifications \rightarrow Zeros and poles.



Let us assume $\frac{N(s)}{D(s)}$, $\# \text{zeros} \leq \# \text{poles} \Rightarrow$ Low Pass

N^{th} order polynomial (with real coefficients)

Even N $\frac{N}{2}$ 2nd order polynomials w/ real coeffs.


Odd N $(\frac{N-1}{2})$ 2nd order + 1 first order, all with real coeffs.

Let us consider Filters of this type : $H(s) = \frac{1}{D(s)}$


$$= \frac{1}{D_1(s) \cdot D_2(s) \cdots D_k(s)} \quad \text{Product of 1st and 2nd order terms}$$

$$= \frac{1}{D_1(s)} \cdot \frac{1}{D_2(s)} \cdot \frac{1}{D_3(s)} \cdot \dots \cdot \frac{1}{D_k(s)} \quad \Rightarrow \text{Cascade!!}$$

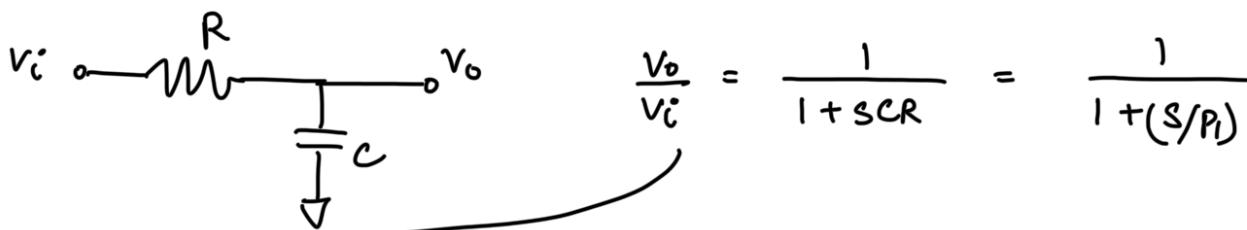First and second order active filters? : (low pass)




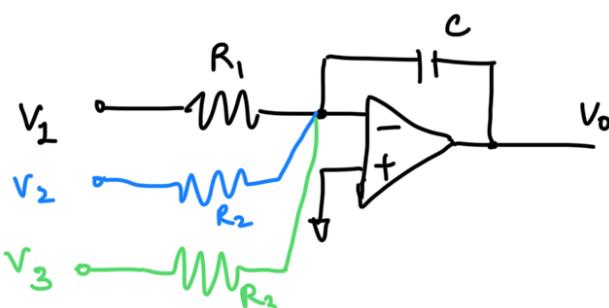
Building block of filters \rightarrow Integrators.




$$V_o = \left(-\frac{1}{sCR_1} \cdot V_1 \right) \left(-\frac{1}{sCR_2} V_2 \right) \cdot \left(-\frac{1}{sCR_3} V_3 \right)$$
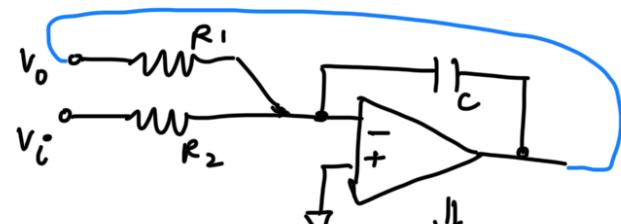
$$(V_o - V_i) \left(-\frac{P_1}{s} \right) = V_o$$



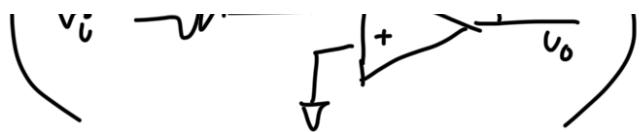


Now:

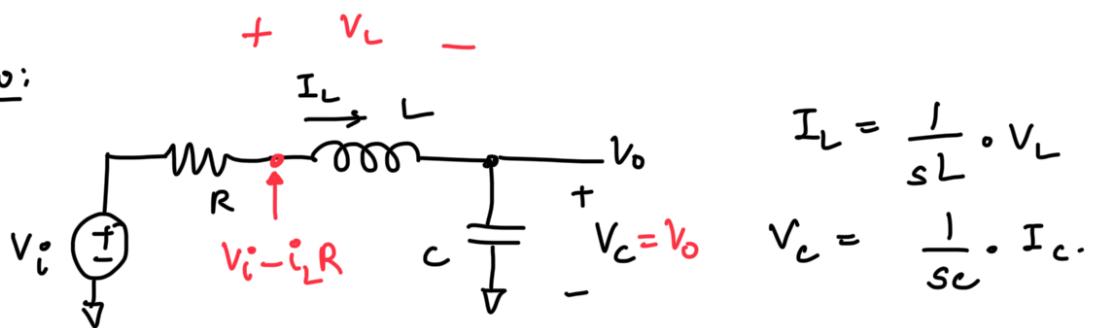


$$V_L = (V_i - i_L R - V_o) \quad \therefore R I_L = \frac{(V_i - i_L R - V_o)R}{sL}$$

$$\text{let } \hat{V}_L = I_L R \quad R \frac{I_L}{sL} = V_o \cdot R$$
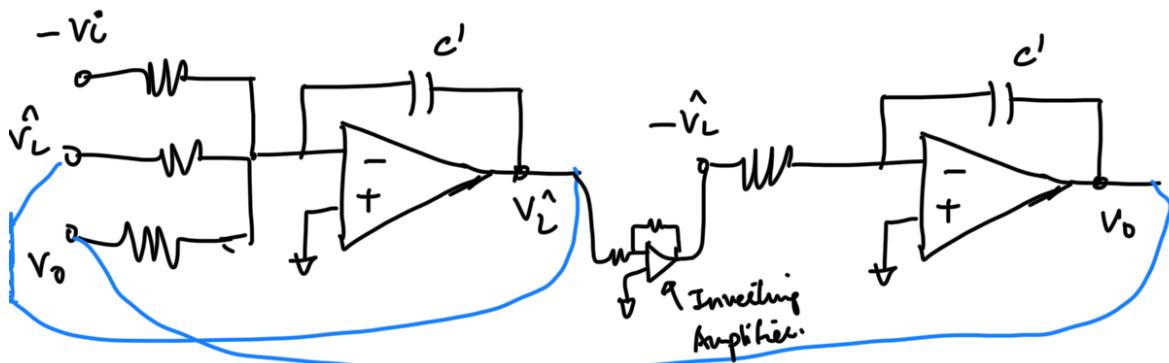
$$\therefore (V_i - \hat{V}_L - V_o) \cdot \frac{R}{sL} = \hat{V}_L ; \quad \hat{V}_L \cdot \frac{1}{sL} = V_o.$$




A Cleaner circuit:

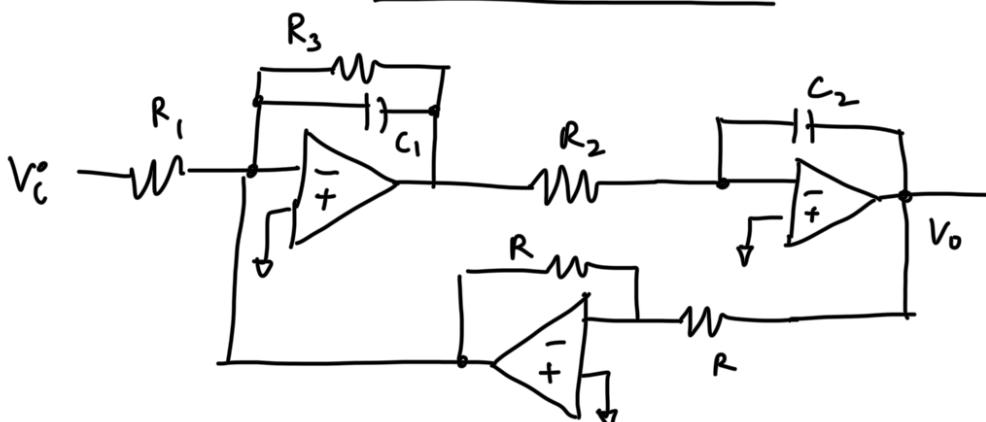


Most general form of a 1st order Transfer function:

$\dots \times \frac{s + \omega_n}{s + \omega_n}$
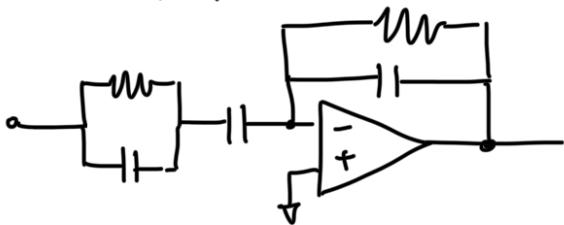
$$H(s) = \frac{b_0 + b_1 s}{a_0 + a_1 s} \quad \text{Bilinear}$$



2nd order filter:

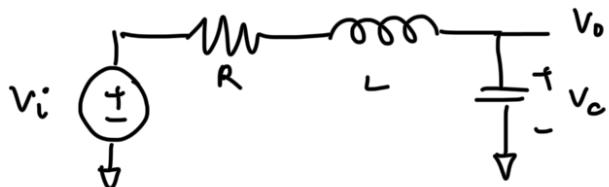


State Variables: I_L, V_C

Active implementation:

Integrator outputs.

N^{th} order: N integrators...
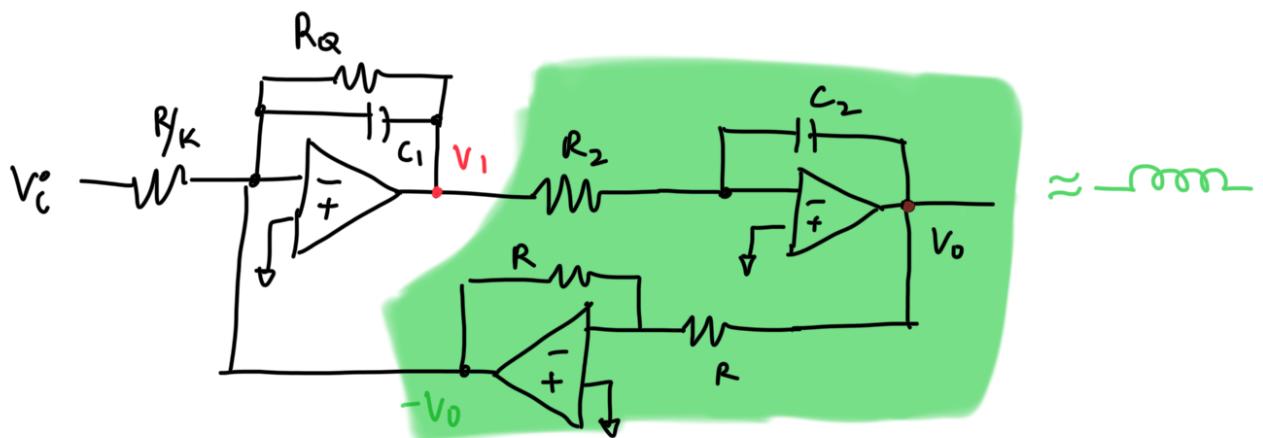
$$RI_L = -\frac{R}{sL}(-V_i + I_L R + V_o) ; -V_o = -\frac{1}{SCR}(I_L R)$$





$$\left(\frac{s}{\omega_n}\right)^2 + \frac{s}{\omega_n Q} + 1 ; \omega_n = \frac{1}{CR} ; Q = R_Q/R.$$

$$V_o = -\frac{1}{SCR} \cdot V_i ; V_i = -\left(\frac{R_Q}{1+SCR}\right)\left(-\frac{V_o}{R} + \frac{kV_i}{R}\right)$$

$$\boxed{\frac{V_o}{V_i} = \frac{k}{(SCR)^2 + SCR \cdot \frac{R}{R_Q} + 1}} \rightarrow \text{Lowpass} ; \frac{R_Q}{R}$$
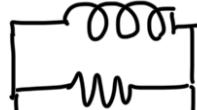
$$\frac{V_i}{V_o} = \frac{-SCR}{(SCR)^2 + SCR \cdot \frac{R}{R_Q} + 1} \rightarrow \text{Bandpass} ; \frac{R_Q}{R} ; \frac{1}{CR}$$



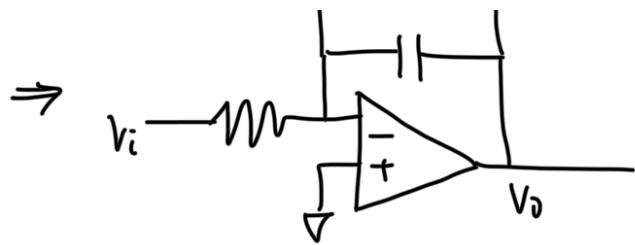

Low Pass :

$$\frac{K}{\left(\frac{S}{\omega_n}\right)^2 + \frac{S}{\omega_n R} + 1}$$

Bandpass :

$$\frac{\frac{K'}{s/\omega_n}}{\left(\frac{S}{\omega_n}\right)^2 + \frac{S}{\omega_n R} + 1}$$

High pass :


$$\frac{\frac{K''}{(s/\omega_n)^2}}{\left(\frac{S}{\omega_n}\right)^2 + \frac{S}{\omega_n R} + 1}$$

Notch / :

$$\frac{K \left(1 + \left(\frac{S}{\omega_n}\right)^2 \right)}{\left(\frac{S}{\omega_n}\right)^2 + \frac{S}{\omega_n R} + 1}$$

Bandstop
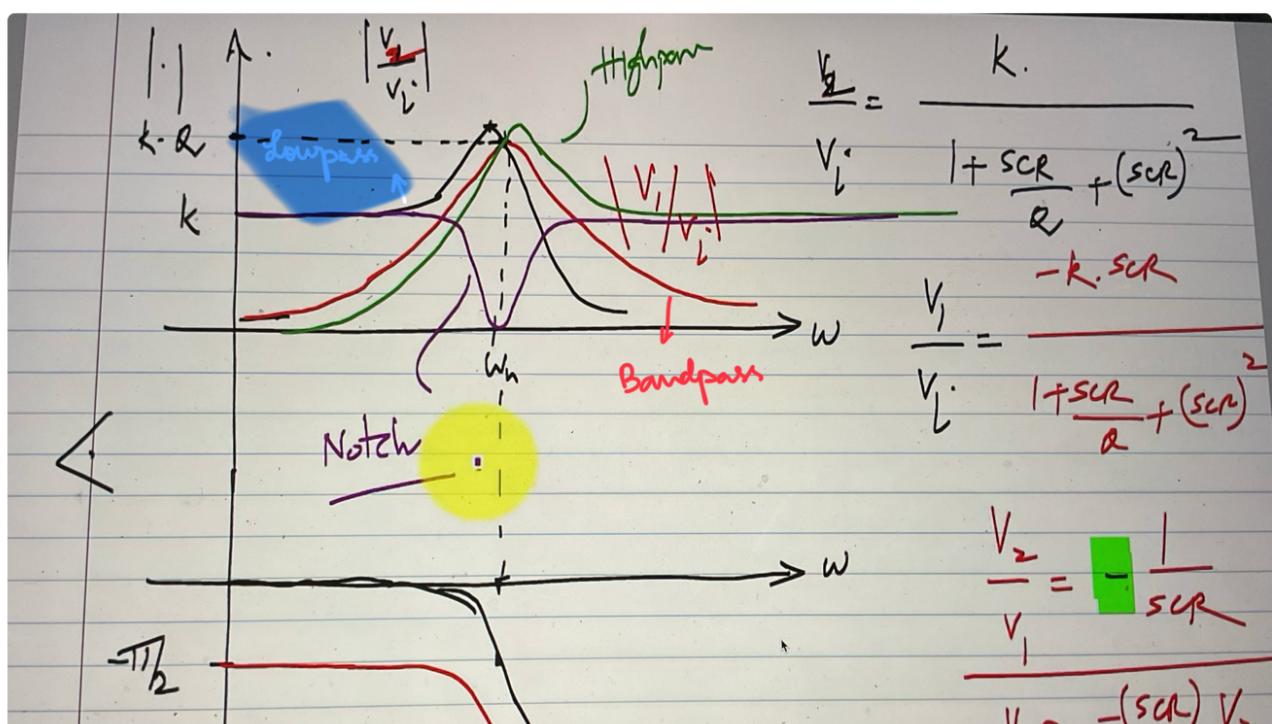
$$\frac{K \left(1 + \left(\frac{S}{\omega_n}\right)^2 \right)}{\left(\frac{S}{\omega_n}\right)^2 + \frac{S}{\omega_n R} + 1}$$





N^{th} order lowpass:


$$H(s) = \frac{1}{1 + a_1 s + \dots + a_N s^N}$$

$$|H(j\omega)|^2 = \frac{1}{1 + c_2 \left(\frac{\omega}{\omega_n}\right)^2 + \dots + c_{2N-2} \left(\frac{\omega}{\omega_n}\right)^{2N-2} + c_{2N} \left(\frac{\omega}{\omega_n}\right)^{2N}}$$

Only even order terms, order $2N$.

o "for maximally flat magnitude"

N^{th} order max. flat magnitude filter $|H(j\omega)|^2 = \frac{1}{1 + \left(\frac{\omega}{\omega_N}\right)^{2N}}$

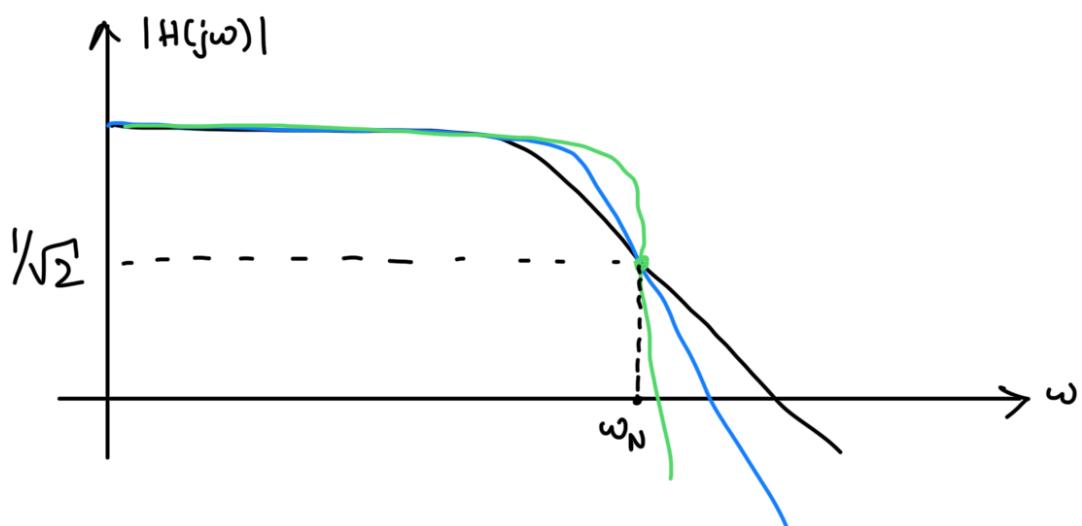

$$H(s) = \frac{1}{D(s)} \quad |H(j\omega)|^2 = \frac{1}{|D(j\omega)|^2} = \frac{1}{1 + \left(\frac{\omega}{\omega_N}\right)^2}$$

Need $D(s)$ such that

$$|D(j\omega)|^2 = 1 + \left(\frac{\omega}{\omega_N}\right)^{2N}$$


$$|D(j\omega)|^2 = D(j\omega) \cdot D^*(j\omega) = D(s) \cdot D(-s) \Big|_{s=j\omega}$$

$$\therefore D(s) D(-s) \Big|_{s=j\omega} = 1 + \left(\frac{s}{j\omega_N}\right)^{2N}$$

Solving for the roots :

$$1 + \left(\frac{s}{j\omega_N}\right)^{2N} = 0 \Rightarrow \left(\frac{s}{j\omega_N}\right)^{2N} = e^{j\left(\frac{2\pi k + \pi}{2N}\right)}$$
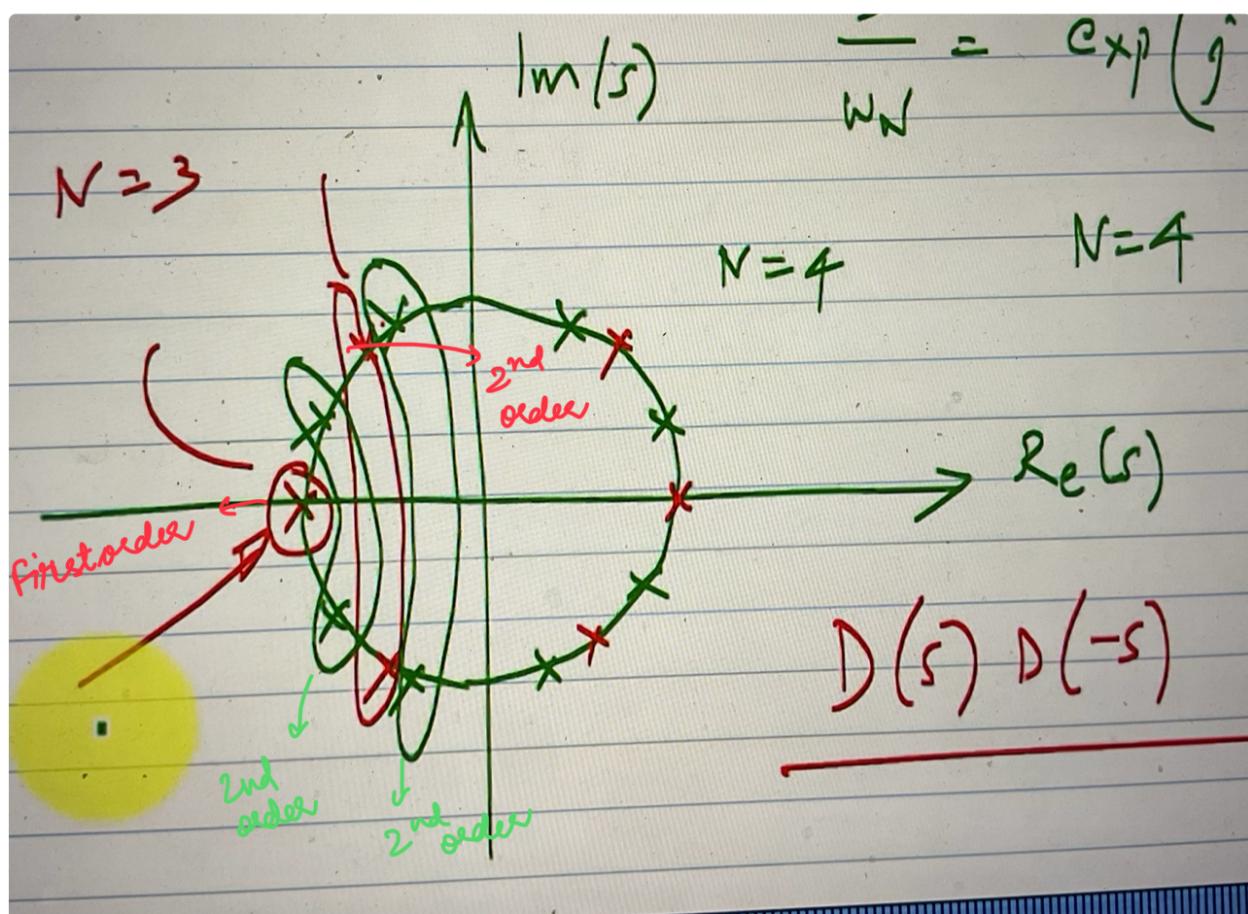
$$\therefore \frac{s}{\omega_N} = e^{j\left(\frac{2\pi k + \pi}{2N} + \frac{\pi}{2}\right)}$$



This filter is called a **Butterworth filter**...

Now, to implement a 3^{rd} order filter, we have to cascade a 1^{st} and a 2^{nd} order filter.

But, what should be the order? 1 then 2? or 2 then 1?


1^{st} order, and 2^{nd} order. Why? This will prevent V_{pp} from

going to $\pm V_{SAT}$.

Ordering of sections:


Increasing order of Q to maximize the input that can be applied (outputs limited to V_{SAT})

Gyrorator:

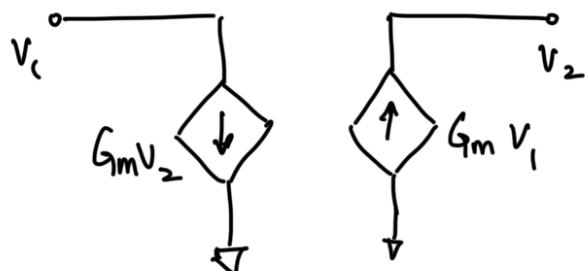

$$\begin{aligned} \text{Capacitor} &\leftrightarrow \text{Inductor} \\ \text{Resistor} &\leftrightarrow \text{Resistor} \\ R \parallel C &\leftrightarrow R \text{ Series } C \\ Z &\leftrightarrow 1/Gm^2 Z. \end{aligned}$$

Gm-C filter:

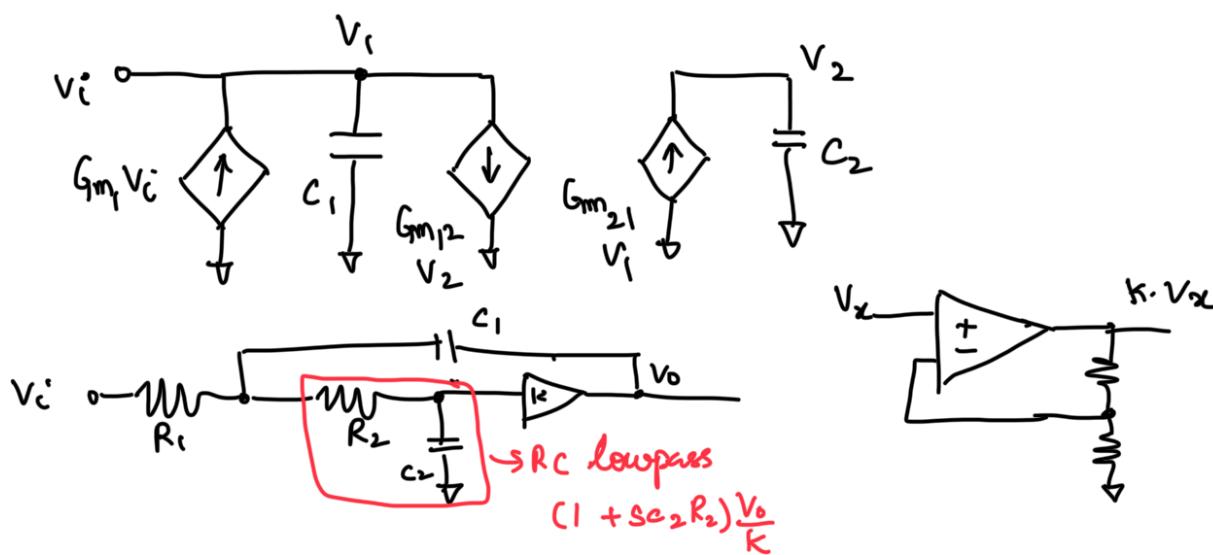


$$\frac{V_o}{V_i} = \frac{V_i - (1 + sC_2 R_2) V_o / K}{R_1}$$

$$= \frac{K}{s^2 C_1 C_2 R_1 R_2 + s[R_1 C_2 + R_2 C_2 + R_1 C_1 (1-K)] + 1}$$

$$\begin{aligned} \text{If } R_1 C_1 &= R_2 C_2, & = & \frac{K}{s^2 C^2 R^2 + sCR(3-K) + 1} \approx \frac{K}{(\gamma \omega_n)^2 + \frac{s}{Q\omega_n} + 1.} \\ R_1 &= R_2 = R \\ C_1 &= C_2 = C \end{aligned}$$


For Real poles Q not greater than 1/2 ! $\circ\circ$

Another one:

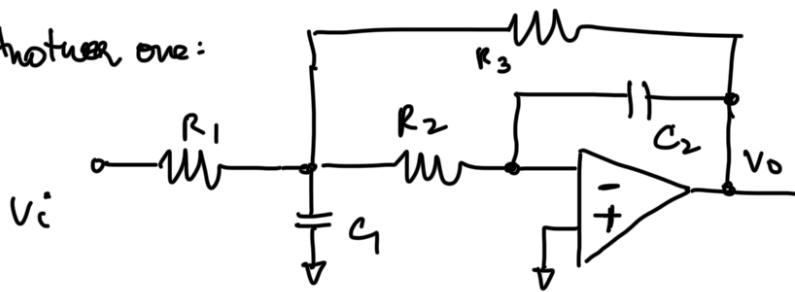


Ranch Filter

Problem:

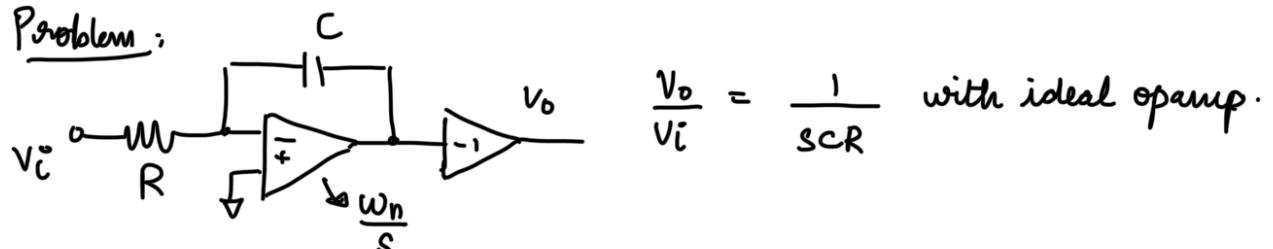
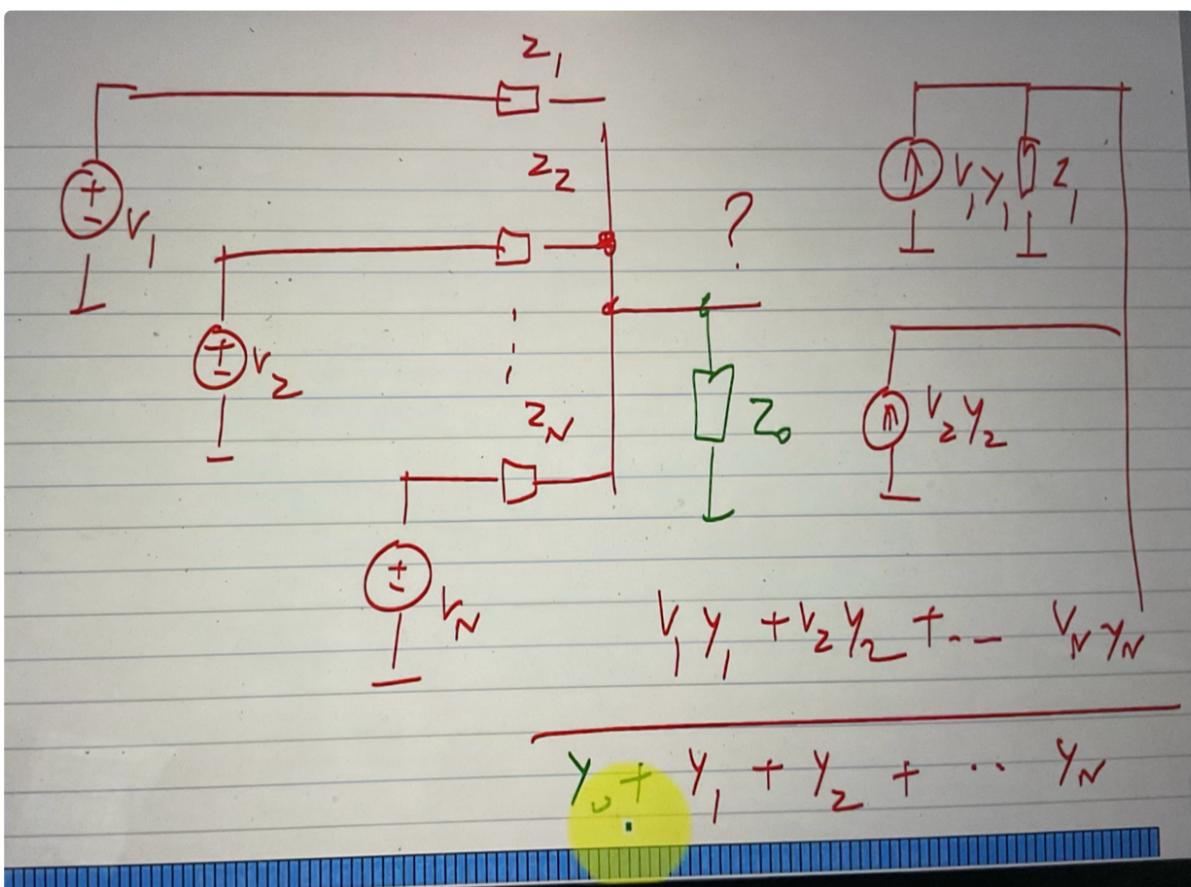
$$V_o = \frac{s}{\omega_n} V_o = \left(\frac{V_i}{R} - V_b sC \right) \frac{1}{R + sC}$$



$$\frac{V_o}{V_i} = \frac{1}{sCR} \left(1 + \frac{s}{\omega_n} + \frac{1}{\omega_n CR} \right)$$

$\omega_n \rightarrow \frac{1}{CR}$

Let's handplot this Transfer function:

