

+ Nagendra Krishnapura Analog Notes

Oscillators

We want natural response decays out in Amplifiers + Filters.

→ We need stability - Forced Response $>$ Natural Response.

But sometimes, we need instability → Oscillators !!


Main place where we need : Clocks + wave generators...

Input for oscillator → None! Except to change frequency.
Just source enough. *Autonomous Circuit*


Utilities of the Oscillators :

- * Clock source - Digital circuits, Sampling
- * (Sineoidal) RF carriers
- * Sineoidal signal sources


Let's dive right in:

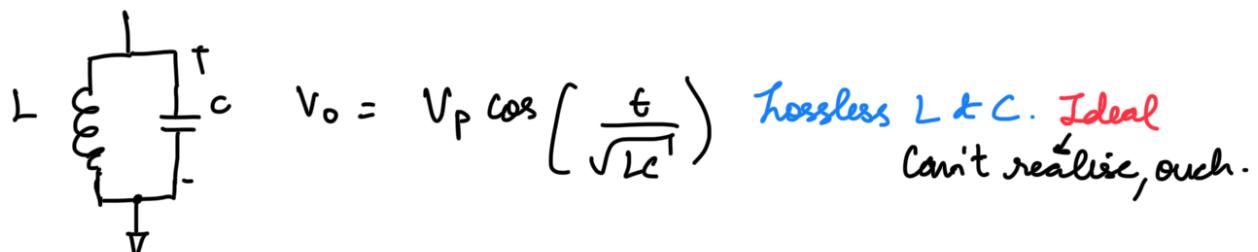

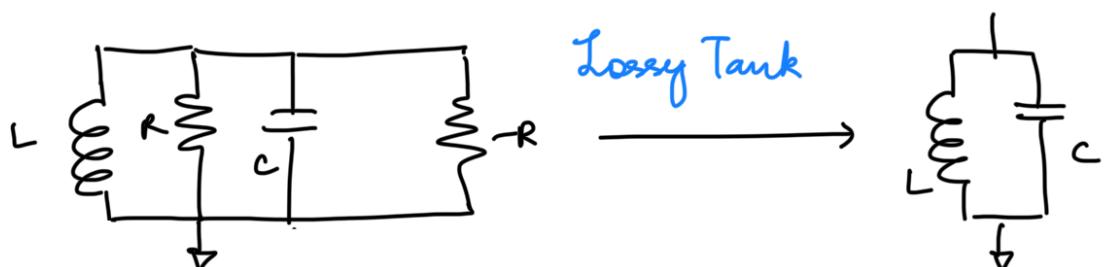Now let us indicate the loss as an R \parallel to LC .




How $-R$?

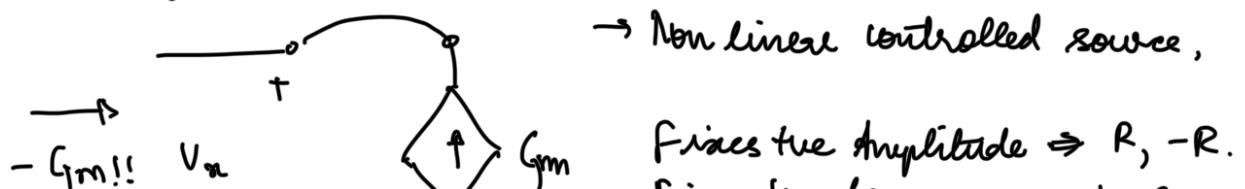



tunes the frequency $\Rightarrow L, C$.

L C Oscillator

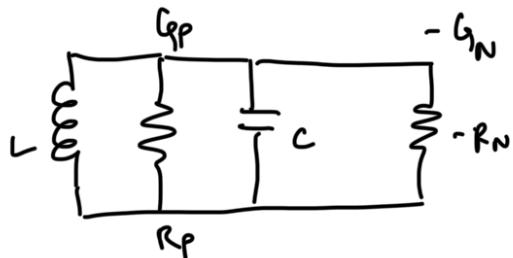




$R_p > 0$ (loss).


Condition for oscillation to start:

$G_N = G_p$: Constant amp.


$G_N > G_p$: Exp. inc. Amplitude

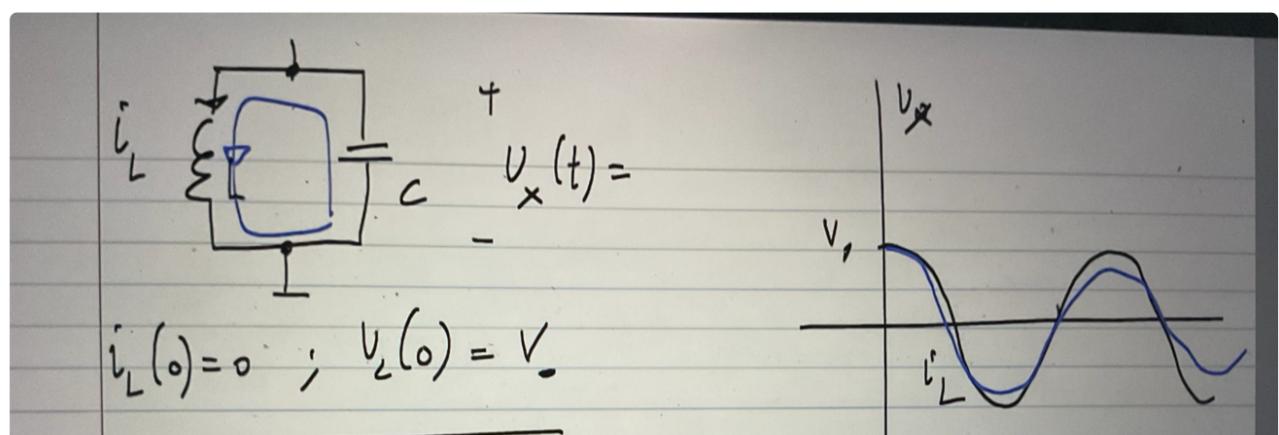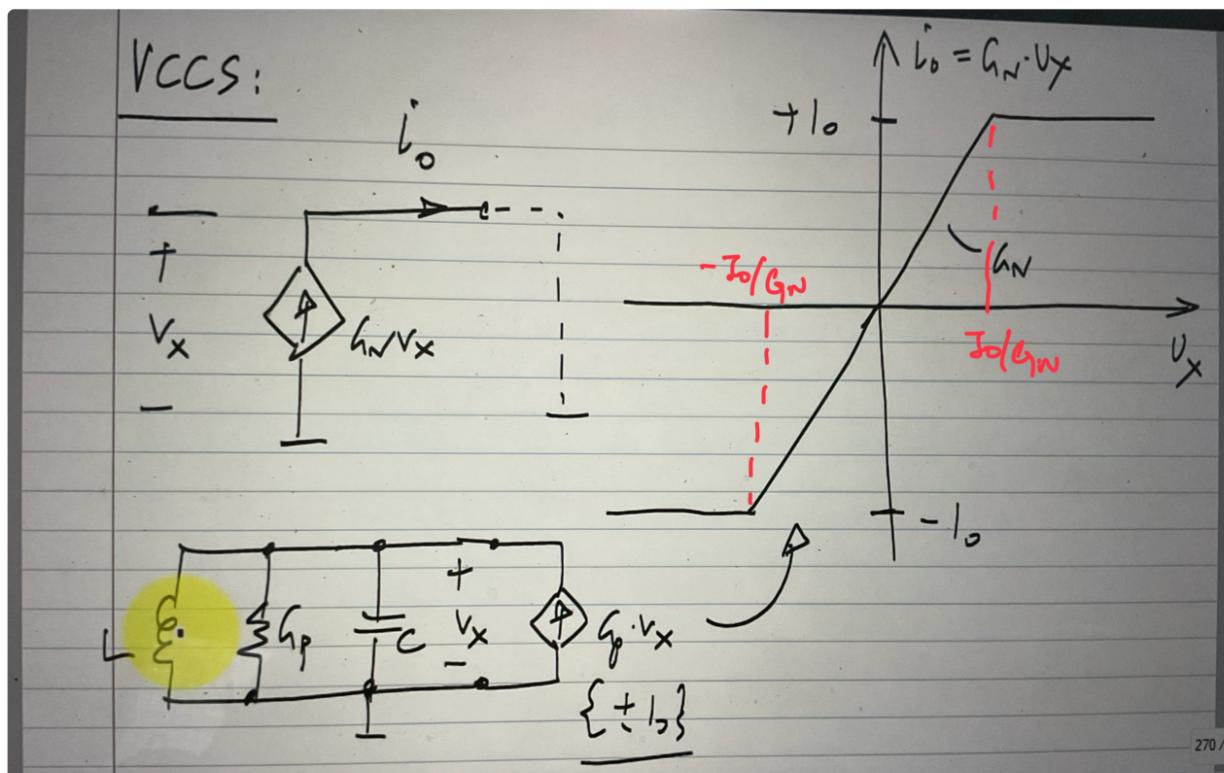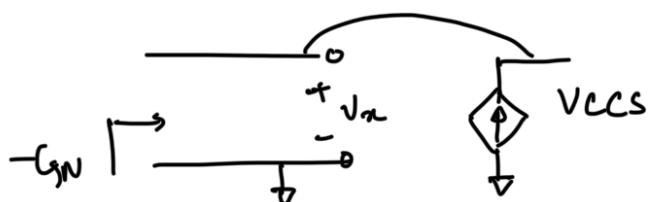$\therefore \underline{G_N \leq G_p} \rightarrow \text{Condition}$.



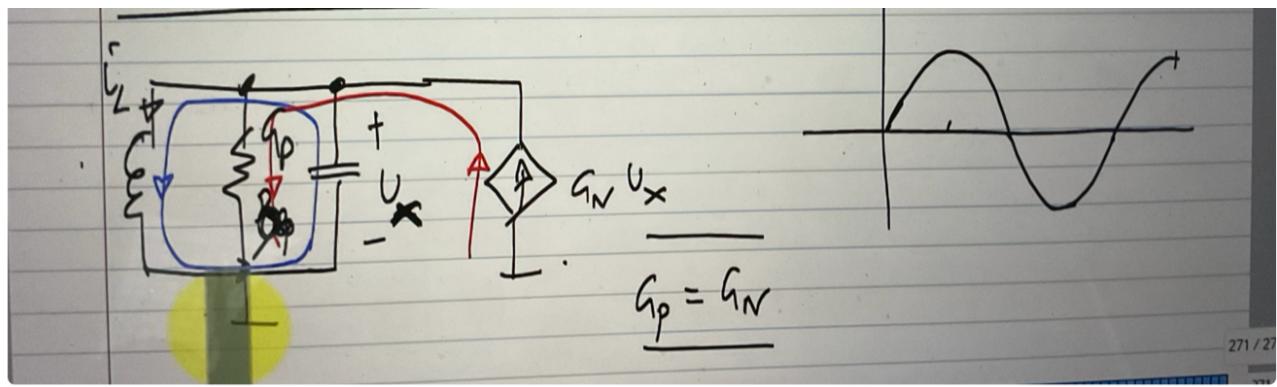


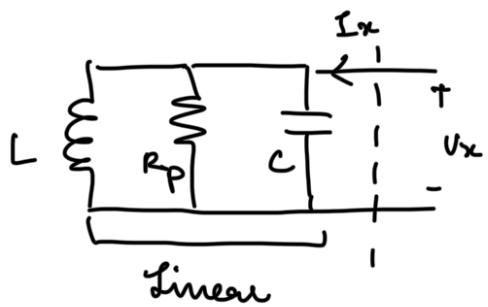\therefore As we can see, in the forced Tank, the amplitude is still dependent on the initial conditions. We'll try to fix that by putting $G_N > G_P$.




$$\frac{V_x}{I_x} = R_P \frac{sL / R_P}{1 + \frac{sL}{R_P} + s^2 LC}$$

Tell's loop plot:

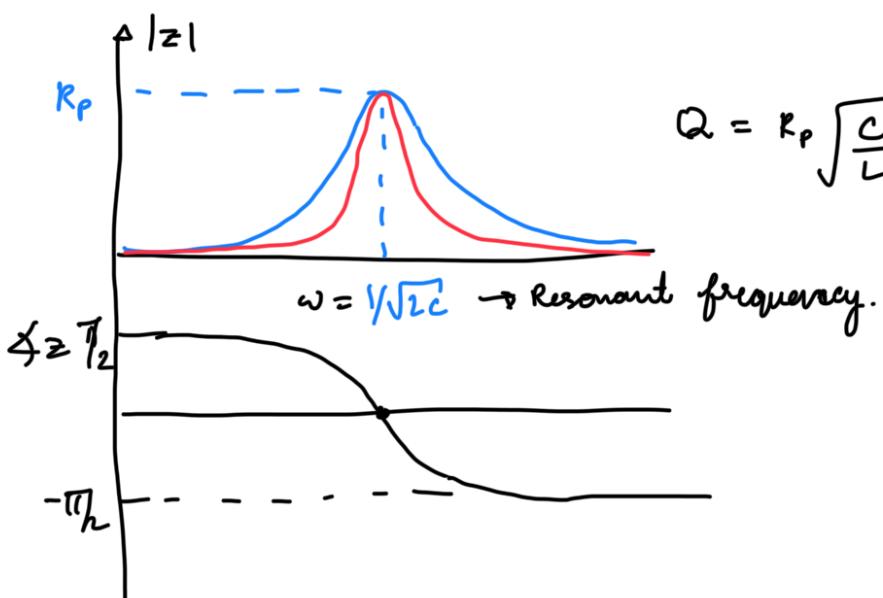



$$Q = R_P \sqrt{\frac{C}{L}}$$

$$\left. \frac{V_x}{I_x} \right|_{\omega=1/\sqrt{LC}} = R_P$$

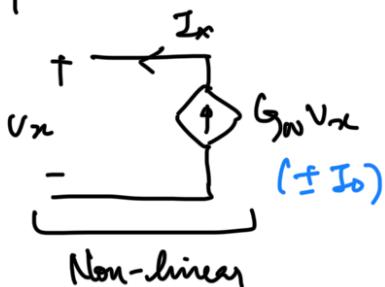

\rightarrow

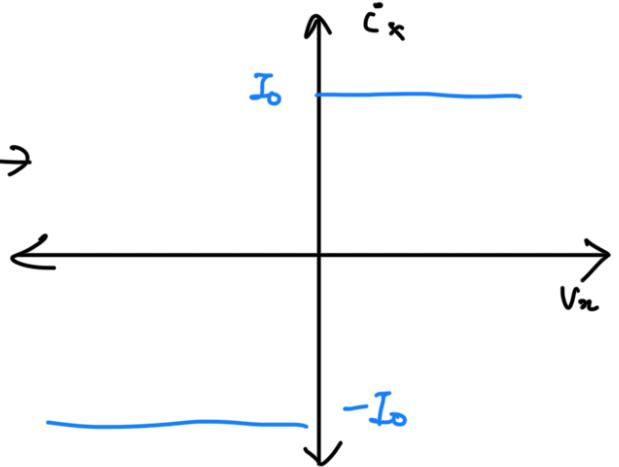

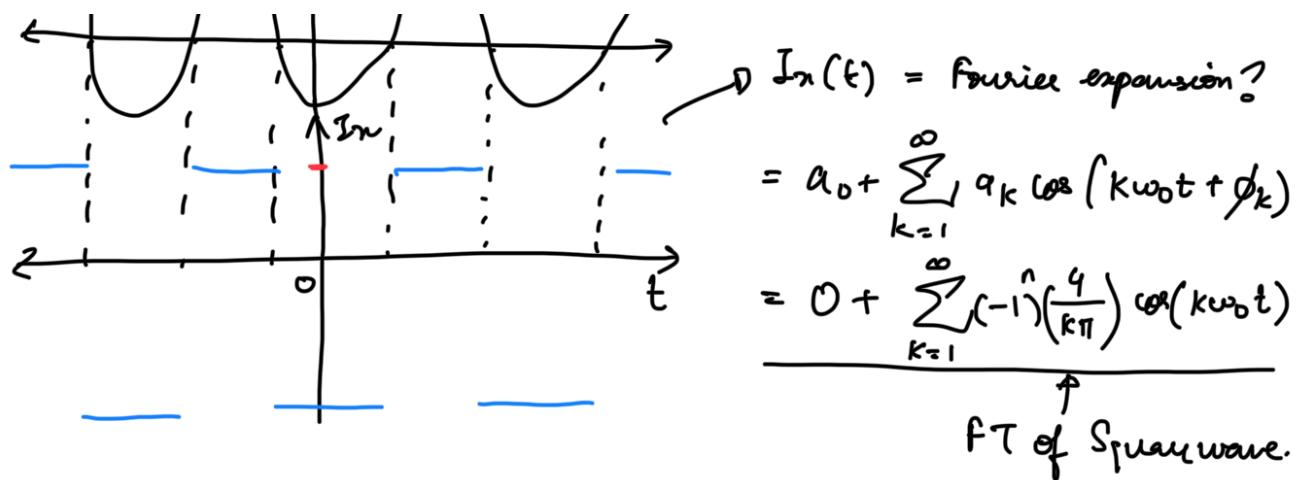

$\therefore V_n(t)$ output of this oscillator = ?

$$V_n = \frac{4 I_0 R_p}{\pi} \cos(\omega_0 t); \text{ Amplitude} : \frac{4 I_0 R_p}{\pi}.$$

High Q \rightarrow Only fundamental voltage exists across the tank.


\rightarrow Tank voltage is of the form $V_p \cos(t/\sqrt{LC})$

Current from G_p : $\sum_k \left(\frac{4 I_0}{\pi} (-1)^{(k-1)/2} \cos\left(\frac{kt}{\sqrt{LC}}\right) \right)$

Fund. component: $\frac{4 I_0}{\pi} \cos\left(\frac{t}{\sqrt{LC}}\right)$

@ $\frac{1}{\sqrt{LC}}$, $\frac{V}{I}$ $\Big|_{\text{tank}} = R_p$; $\frac{4 I_0}{\pi} R_p = V_p$.

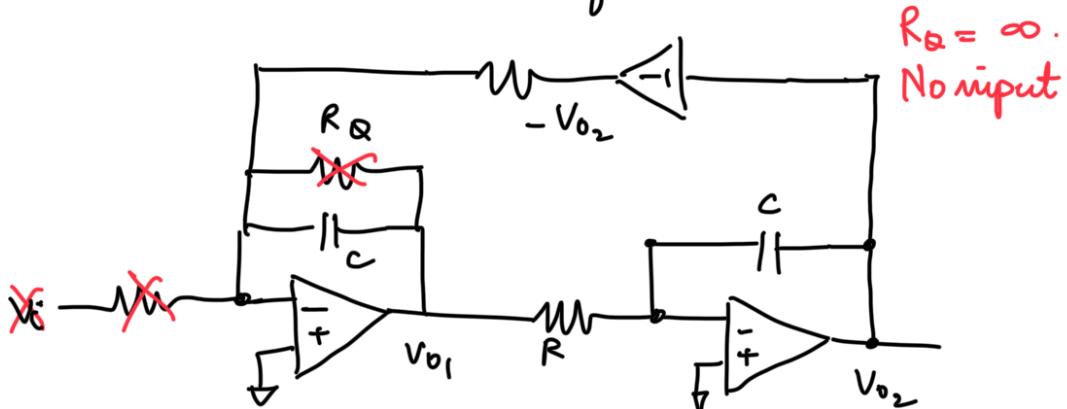How to turn a 2nd order filter as an oscillator?




$$V_{o1} = \frac{1}{sCR} V_{o2}; \quad V_{o2} = -\frac{1}{sCR} V_{o1}$$

Double integrator

oscillator


This is very close to:

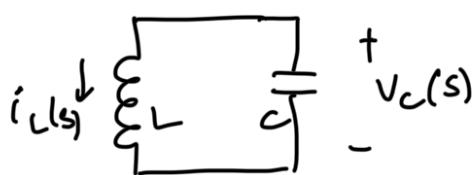


$$i_L(s) = \frac{1}{sL} \cdot V_C(s)$$

$$V_C(s) = -\frac{1}{sc} i_L(s)$$


Now, what if I break the loop here:


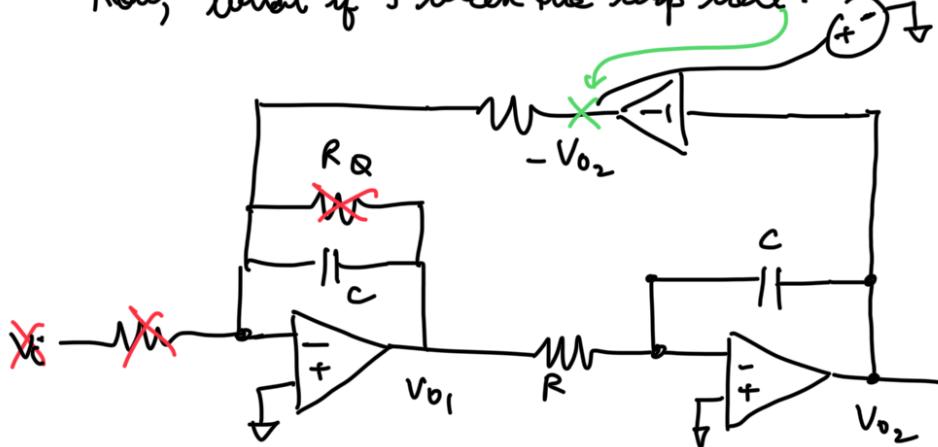

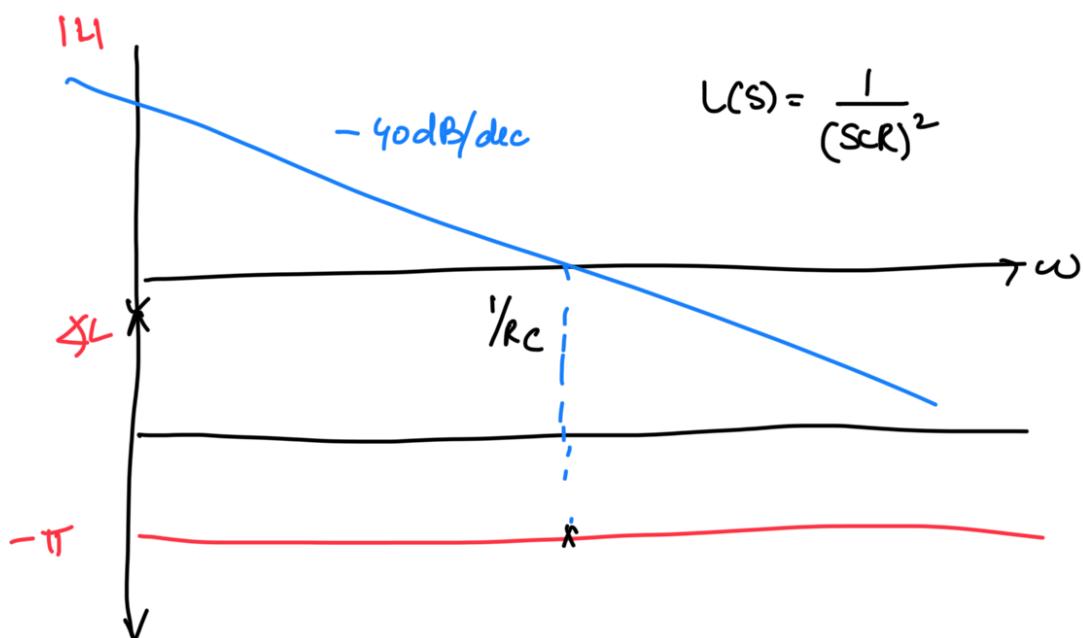
$$\therefore V_{\text{return}} = \left(\frac{1}{sCR}\right)^2 V_{\text{feed}} \quad \therefore \left(\frac{1}{sCR}\right)^2 \rightarrow \text{Bode Plot this}$$




Consider this:

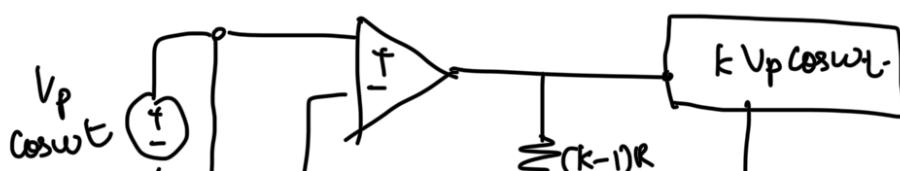


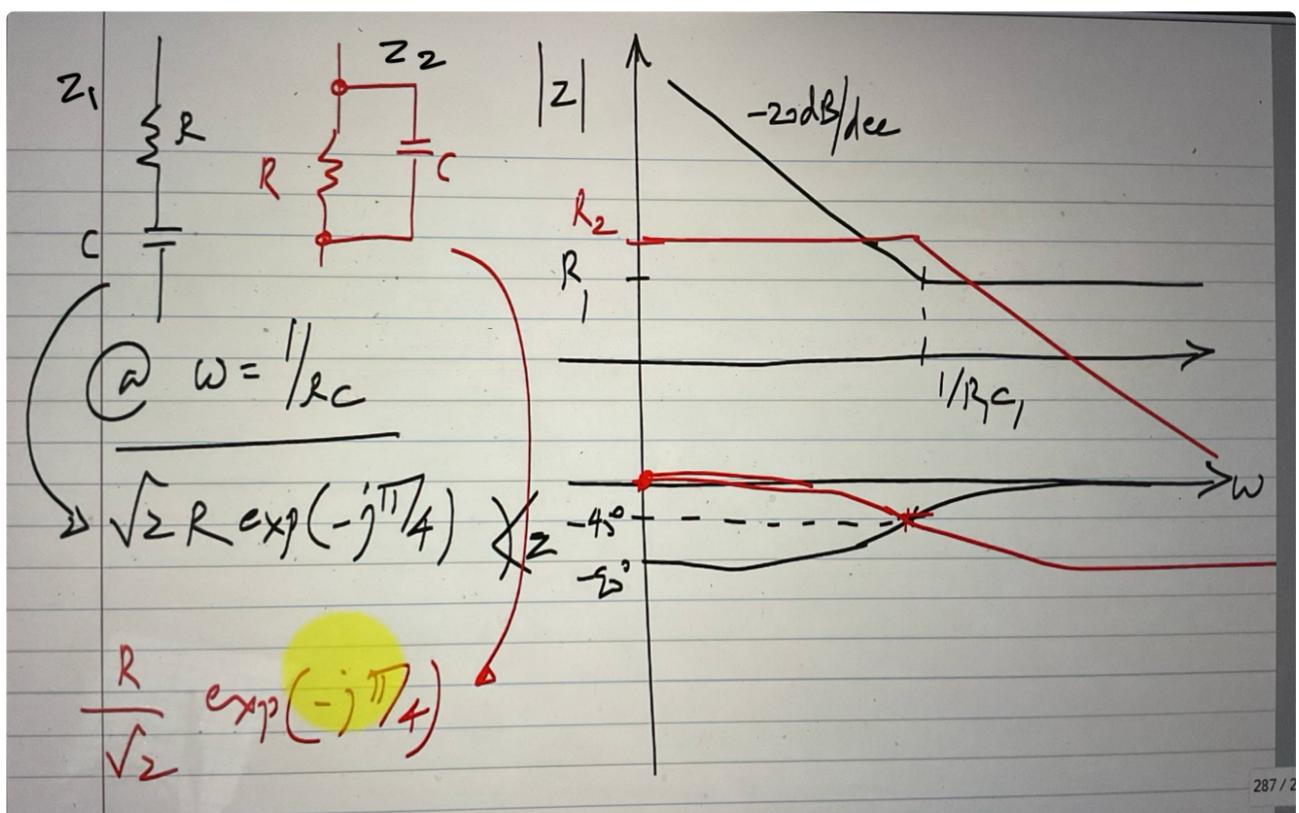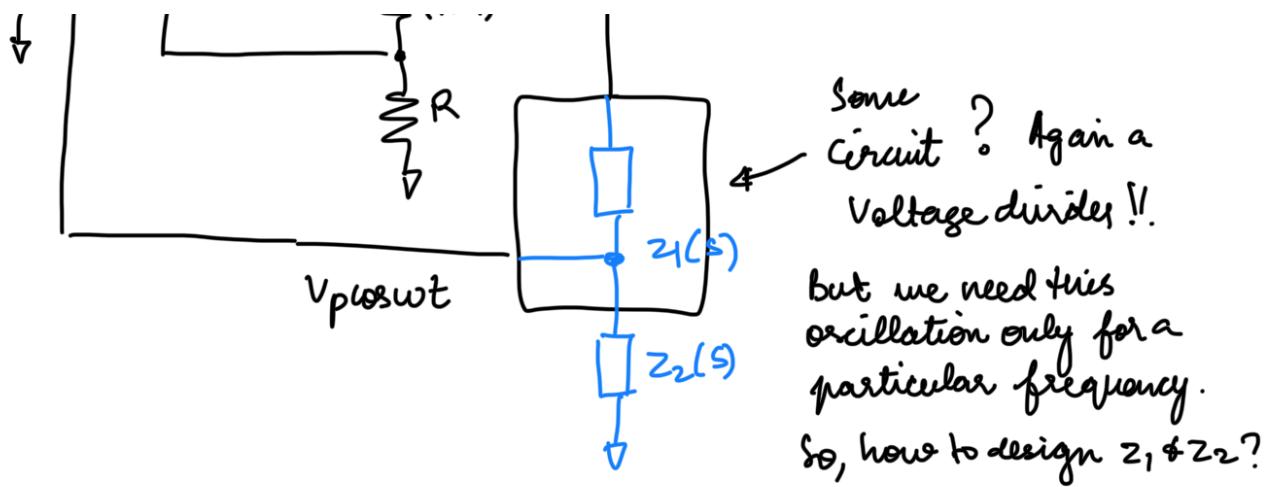


$$k = \frac{z_1}{z_1 + z_2} \Rightarrow \frac{1}{3} \quad [\text{if } R \text{ & } C \text{ are equal in } z_1 \text{ & } z_2].$$

Wien Bridge Oscillator

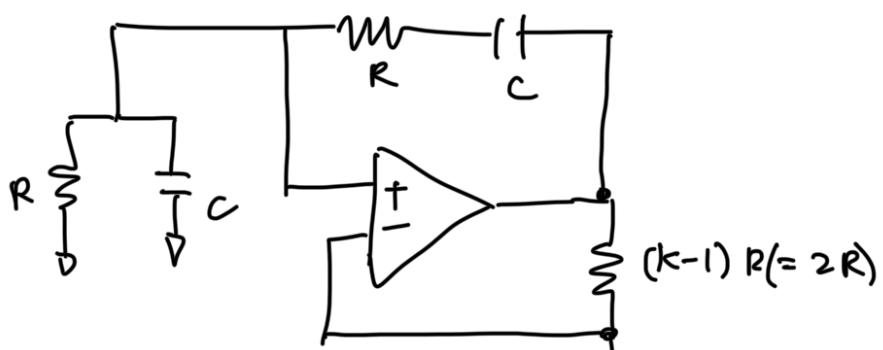

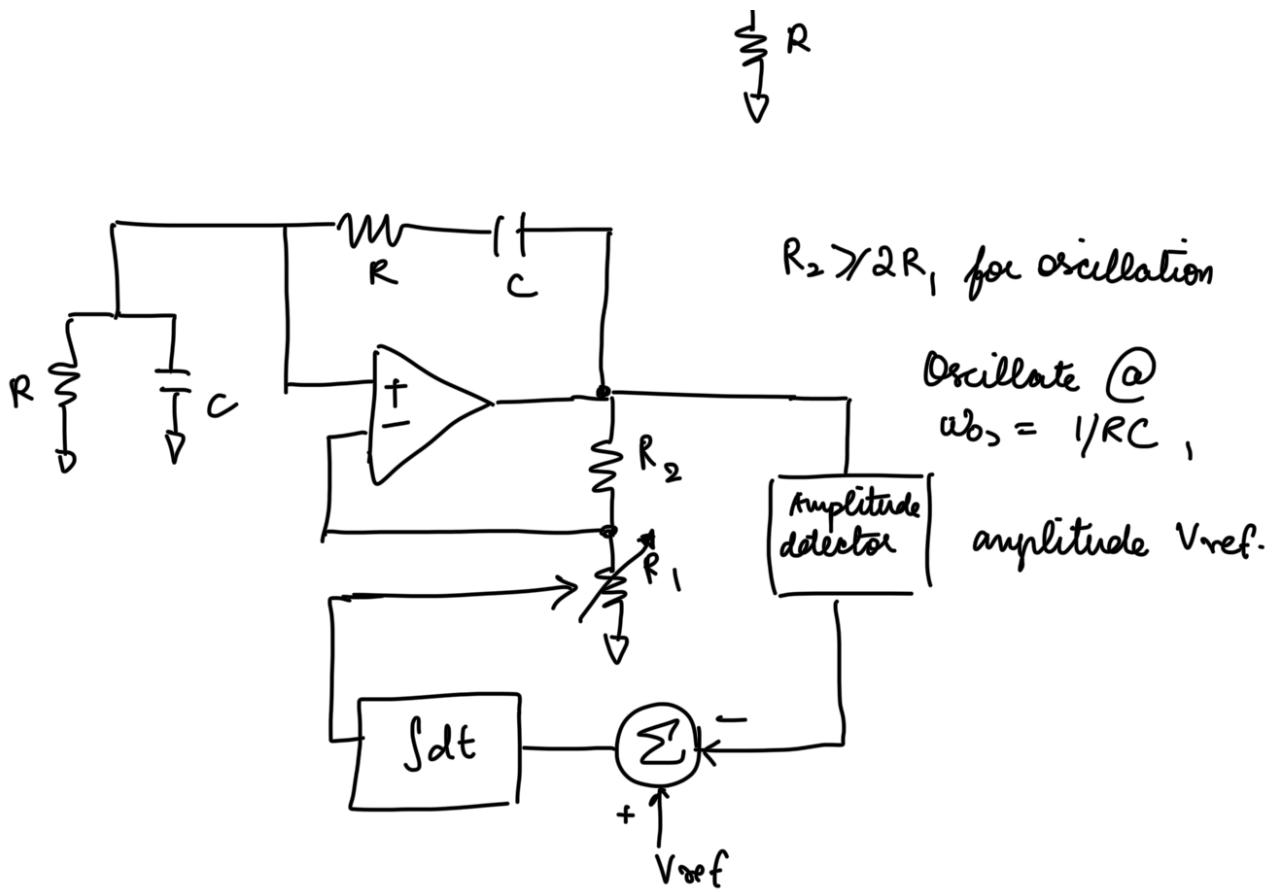


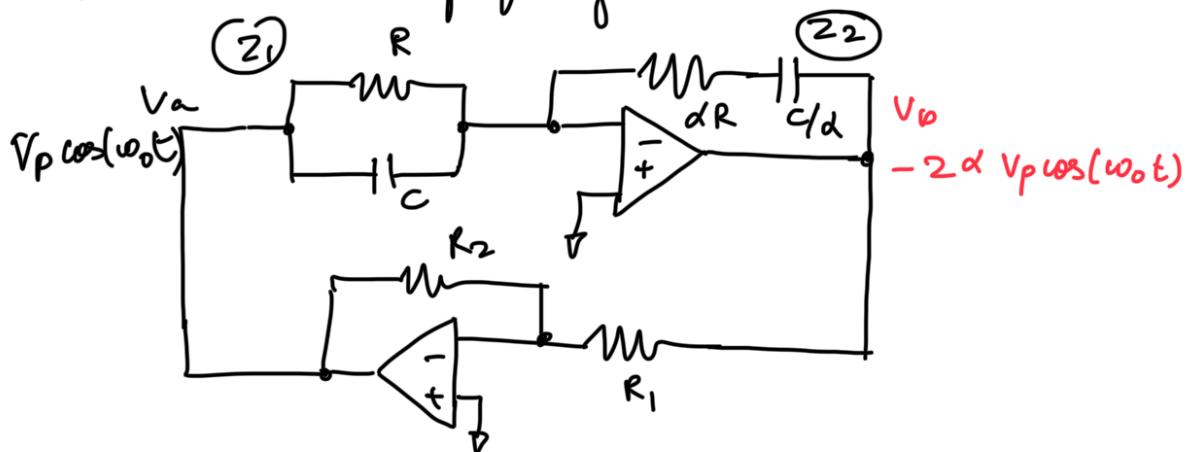
Now consider this frequency selective circuit:





$$\frac{V_b}{V_a} = -\frac{Z_2}{Z_1}; \quad \text{at } 1/RC \Rightarrow -2\alpha, \quad \frac{R_2}{R_1} = \frac{1}{2\alpha}.$$

Flip Z_1 & Z_2 's position: R (Z_1)

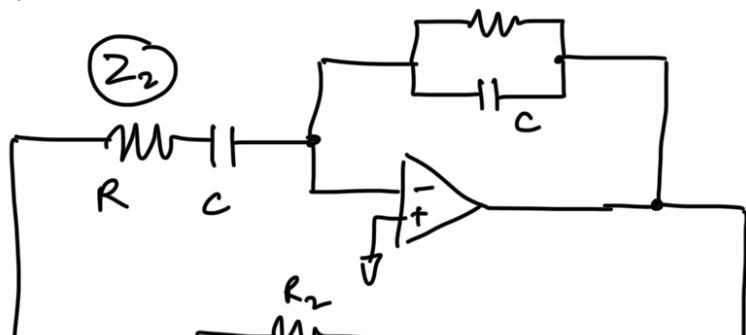

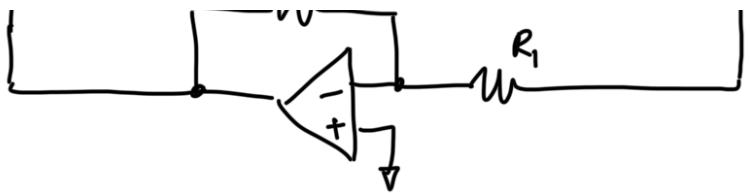

See this new one:

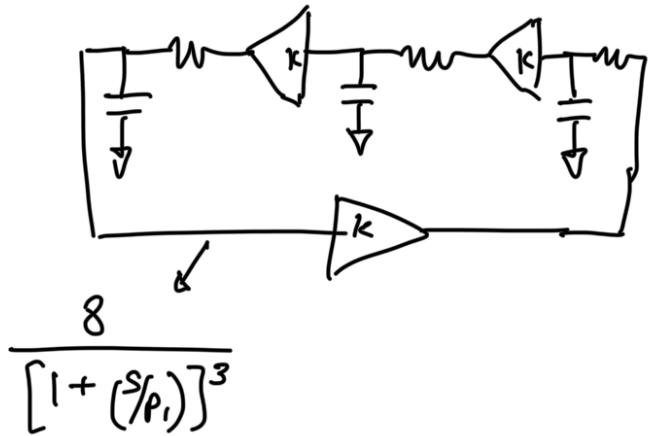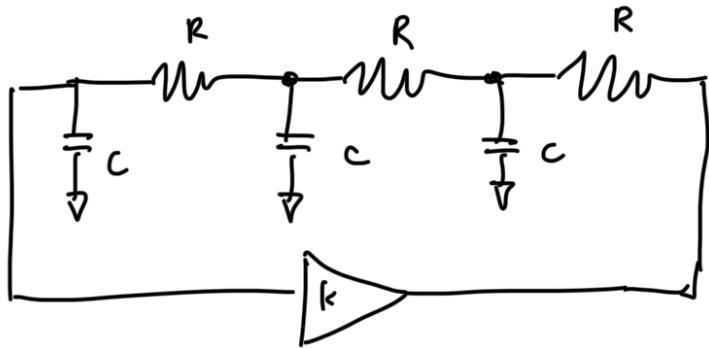

Oscillators:

- LC : Very "good" periodicity.
- Ring oscillators
- Harmonic Oscillators
 - Double integrator ('opamp')
 - Wien Bridge
- Relaxation Oscillators : Schmitt trigger oscillator.