
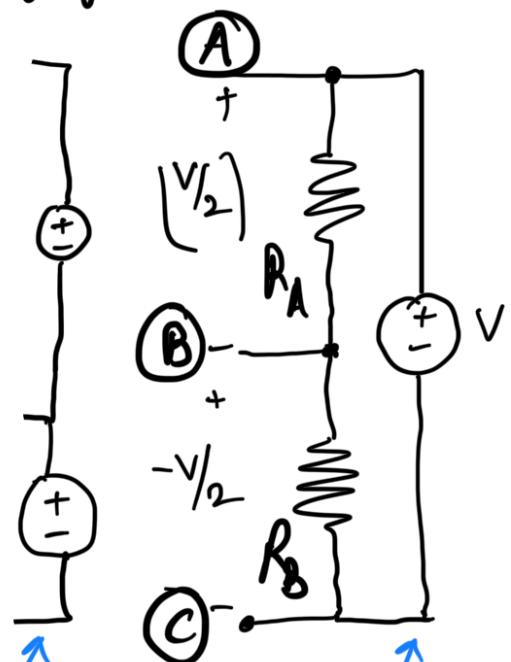


Nagendra Krishnapura Analog Notes - 2

Dual supply and single supply operation of Op-Amps.

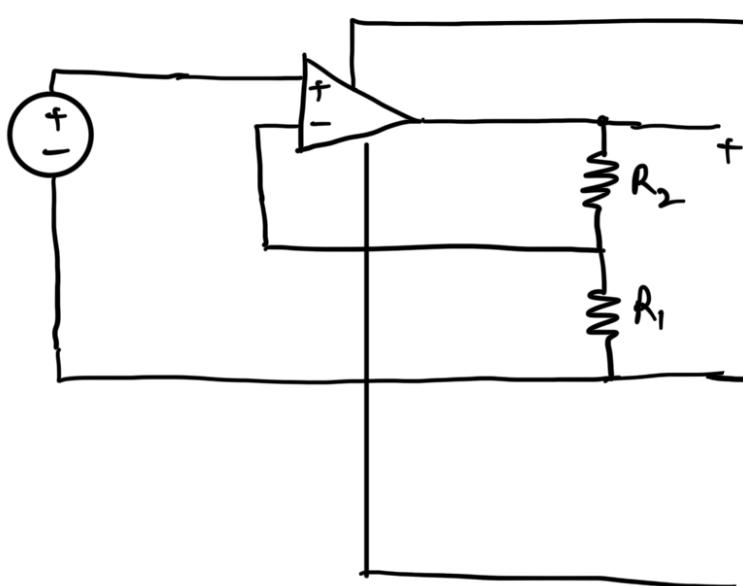How to simplify the Non-inverting Amplifier? [Instead of using two sources (V_{dd} & V_{ss}), trying to use just one source? :



[In practical purposes, when we are looking at bits and pieces of a circuit, we must make sure that the 2-terminal components have one terminal grounded.]

Issue with the Voltage divider shown above (using 2 resistors) is that:

$$V_{AB} + V_{BC} \text{ changes when current is being drawn from it.} \rightarrow V_{AB} = \frac{V}{2} - \Delta I \cdot \frac{R_o}{2} \quad (\text{Thenevin Equivalent})$$

Even to tackle this problem, let's say, R_o must be very small as compared to V .

↓
But this poses another problem! → If R_o is very small, then the current through A-B-C will be much larger

than the current drawn by the Op-Amp - Not useful.

Hence, this solution is not acceptable.

What shall we do? →


$$\text{v}_o = \frac{+}{r} C \rightarrow \infty !!$$

Now, another problem that we have is that, The grounds must be matched properly.

Since v_i is now $v_{i'}$, if we are shifting one ground from B to C [Refer above diagram], We have to add v_{BC} to v_i .

Umm, again adding a Voltage source? Bro - we started out "decreasing" the number of sources!

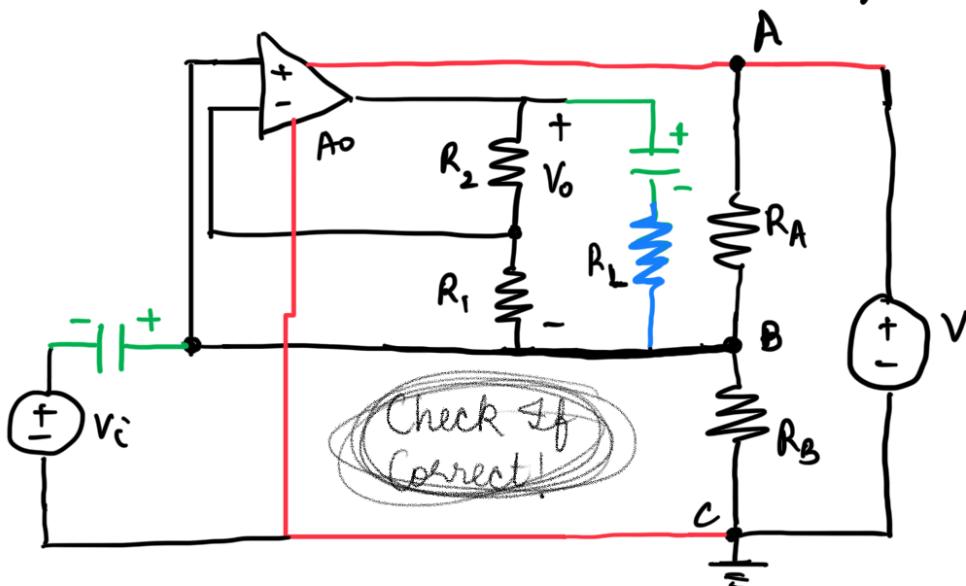
Oh dear, this is where our Capacitor comes!



$$\text{let } V = 24V \\ \therefore V_{AB} = V_{BC} = 12V.$$

This circuit works for
 $v_i = \text{sinusoid},$
 $\omega \gg CR_1/2$

AC Coupling Circuit

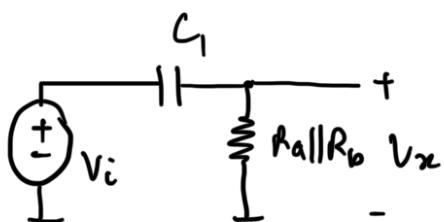

↑ High Pass Filter.

$$\frac{V_o(s)}{V_i(s)} = \frac{s C_1 (R_a || R_b)}{1 + s C_1 (R_a || R_b)}$$

High pass how? \rightarrow At high frequencies, Magnitude should be 1 and phase should be zero.

Here that's the case!!

So, if we have $V_i = \cos(\omega_i t)$, we must choose such that
 $\omega_i \gg \frac{1}{C_1(R_a \parallel R_b)}$ (pole)

Choose corner frequency to be much smaller than the frequency of the sinusoid.

Now, if we want to operate over a range of frequencies
 Make sure the lowest frequency is much larger than the pole.

This involves many components and less constraints.)

This means we need to have some intuition or experiment A LOT to arrive at a particular set of values for C_1 , R_a & R_b .


For instance, $\omega_i \gg \frac{1}{C_1(R_a \parallel R_b)}$.

$$\Rightarrow C_1 \gg \frac{1}{\omega_i (R_a \parallel R_b)} . \rightarrow \text{If } \omega_i \rightarrow \infty, C_1 = 10 \text{ or } 100 \text{ nF.}$$

If we do this, then $\omega = \frac{10}{C_1 (R_a \parallel R_b)} \dots$

Substituting & Evaluating the Transfer Function:
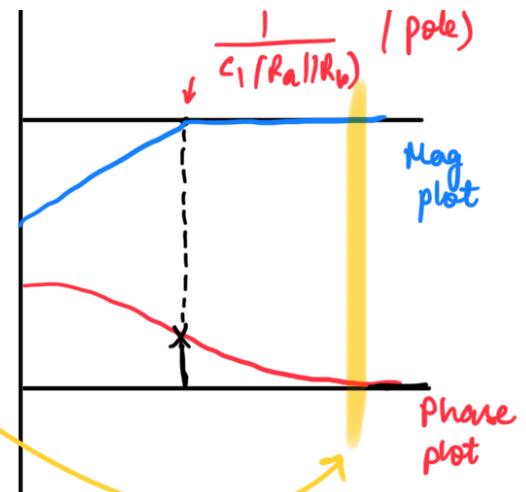
$$C_1(R_a \parallel R_b) \left(j \times \frac{10}{C_1(R_a \parallel R_b)} \right) / \left(1 + j \frac{10}{C_1(R_a \parallel R_b)} \times \cancel{C_1(R_a \parallel R_b)} \right)$$



$$= \frac{10j}{1+10j} = 0.995 \angle 5.7^\circ$$

↑ ↑
Close to 1 Close to zero.

→ Choose ω to be 20 or 30 times, or even 100 times.

$$= \frac{100j}{1+100j} = \frac{100j(1-100j)}{1^2 - (100j)^2} = \frac{100j + 10^4}{10001}$$

$$= \frac{100}{101}j + \frac{10000}{101} = 1 \angle 0.5729^\circ //$$

YaaaY!!


$\frac{V_c}{V_i}$ (instead of Resistor Voltage, capacitor Voltage)

= Mag will be very close → Behaves as a short when compared to resistor.

↓

This means, there is some change in the voltage, but it is so small that we neglect it.

Now the circuit has emerged to this.

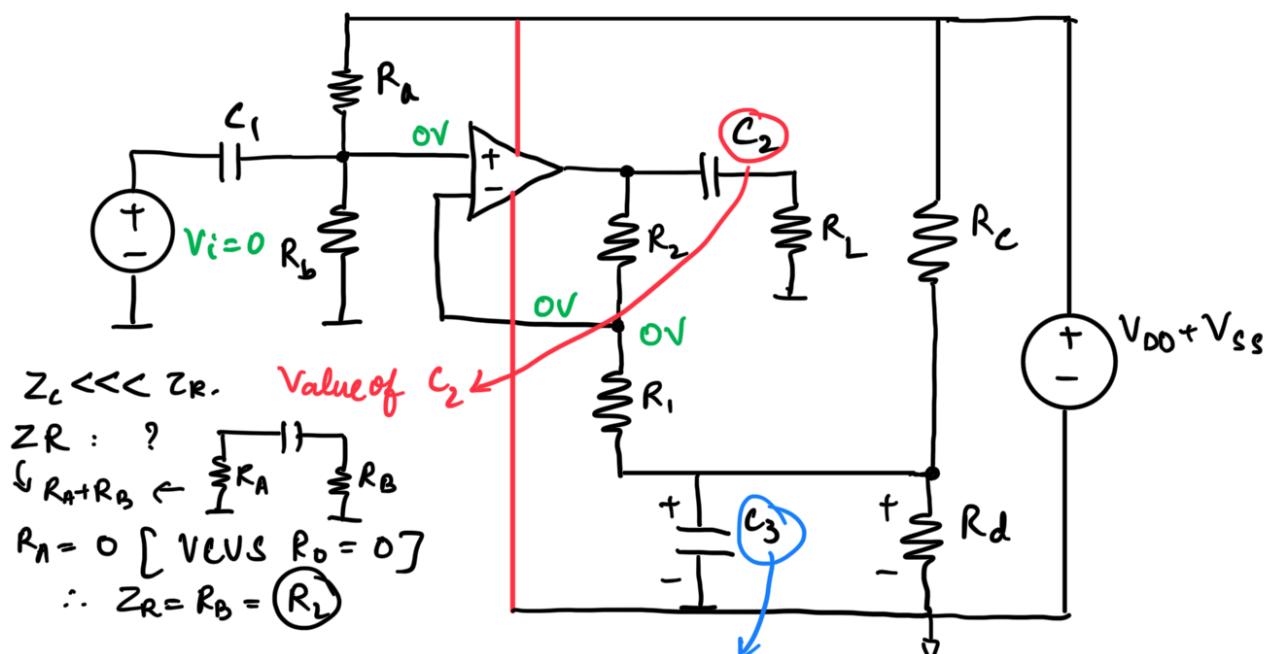

We can reduce it to a ← Value of C_3 ?
 Capacitor in parallel with a Resistor as this is 1st order.
 $\downarrow Z_c \ll Z_R$.

$$R_y = R_c + R_d$$

$$R_x = R_1 \rightarrow \text{How?}$$

$$\frac{1}{\omega C_3} \ll R_1 \parallel (R_c + R_d)$$

Large.

$$R_x \parallel R_y$$

This is known as Level shifting [Adding voltage to input signal]
 $\approx (1/2 V_T)$

Now let's see Where is the Biasing (operating) point.

In the above diagram,

Not very clear...

C_1 & C_2 : ac coupling capacitors (or dc blocking)

C_3 : Bypass capacitor.


at DC point.

Bias/ operating point of Op Amp

Basically, the voltage of input (and output) of the Op Amp when no V_i is connected, and only the Op Amp supplies are connected.


We were keen on making a non-inverting amplifier from a dual supply to a single supply.

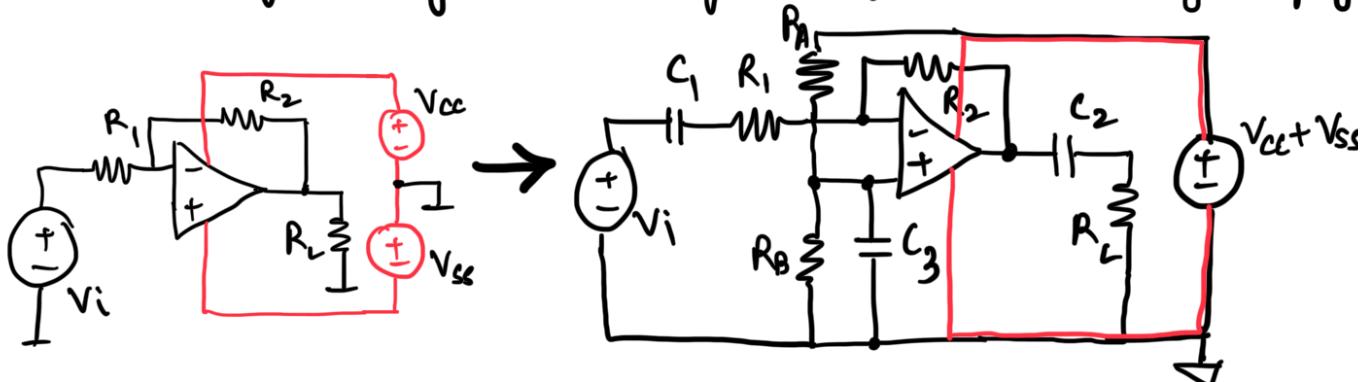Now let's try making an inverting amplifier work on single supply




$$C_1: \frac{1}{\omega_1 C_1} \ll R_1 ; C_2: \frac{1}{\omega_2 C_2} \ll R_2 ; C_3:$$

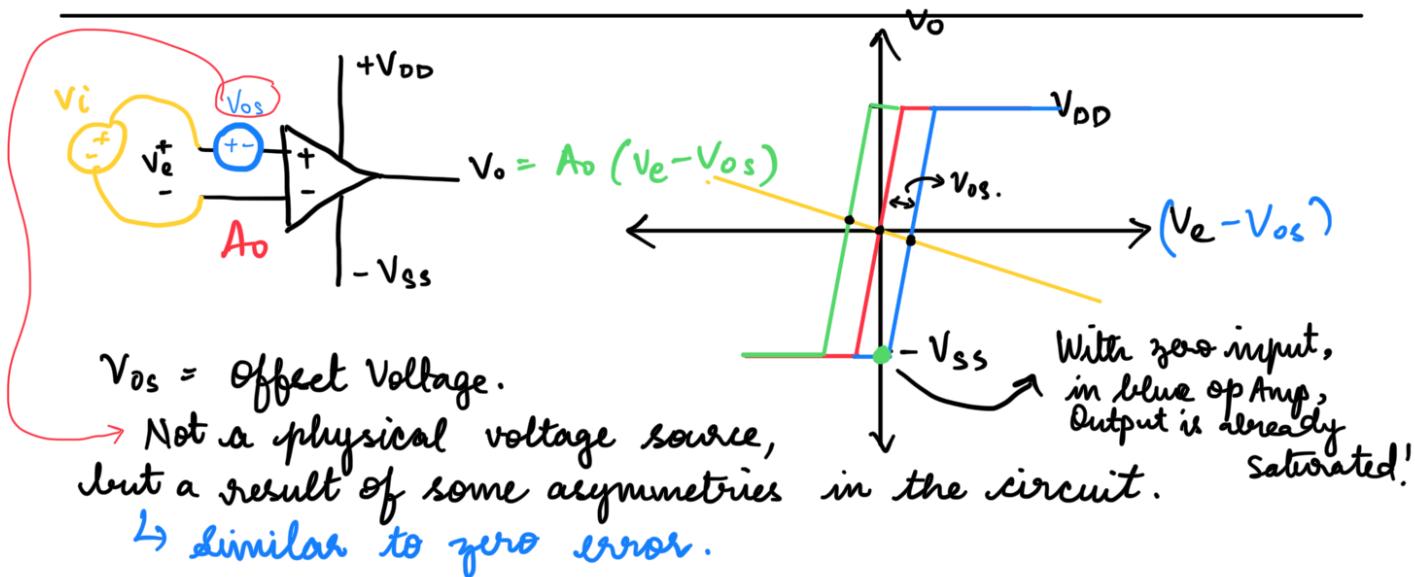Active feedback : Only for DC, not for AC.



V_{os} : random : Gaussian distribution, centered at zero.

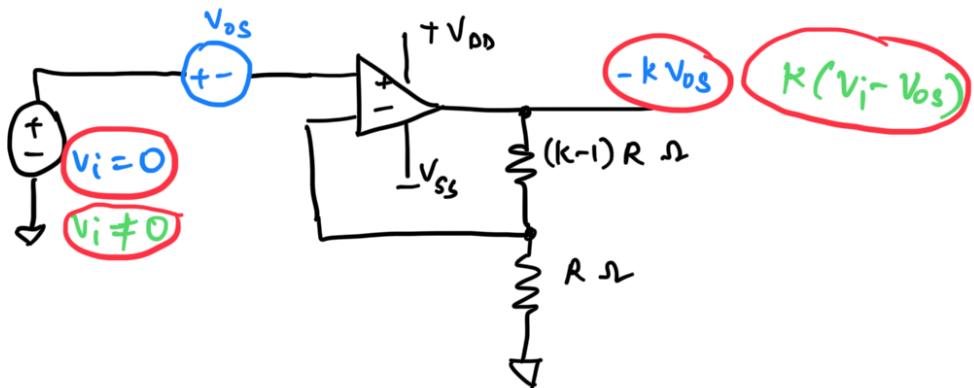Let's take our good old Non-inverting amplifier



Now, By doing KVL and KCL, We get the v_o in terms of v_e .


v_o vs v_e having A_o as the slope is the Op Amp's characteristics.

$v_o = -k v_e$ is the output of the whole circuit. [I.e., the negative amplifier.]

* Op Amp has a built-in offset (modelled by a voltage source in series with the input)

$$\left(\frac{1}{\sqrt{2\pi}} e^{-x^2/2\sigma^2} \right) \quad 3\sigma \rightarrow 99.9\% \quad \sigma \rightarrow 65\text{mV}$$

random, gaussian.

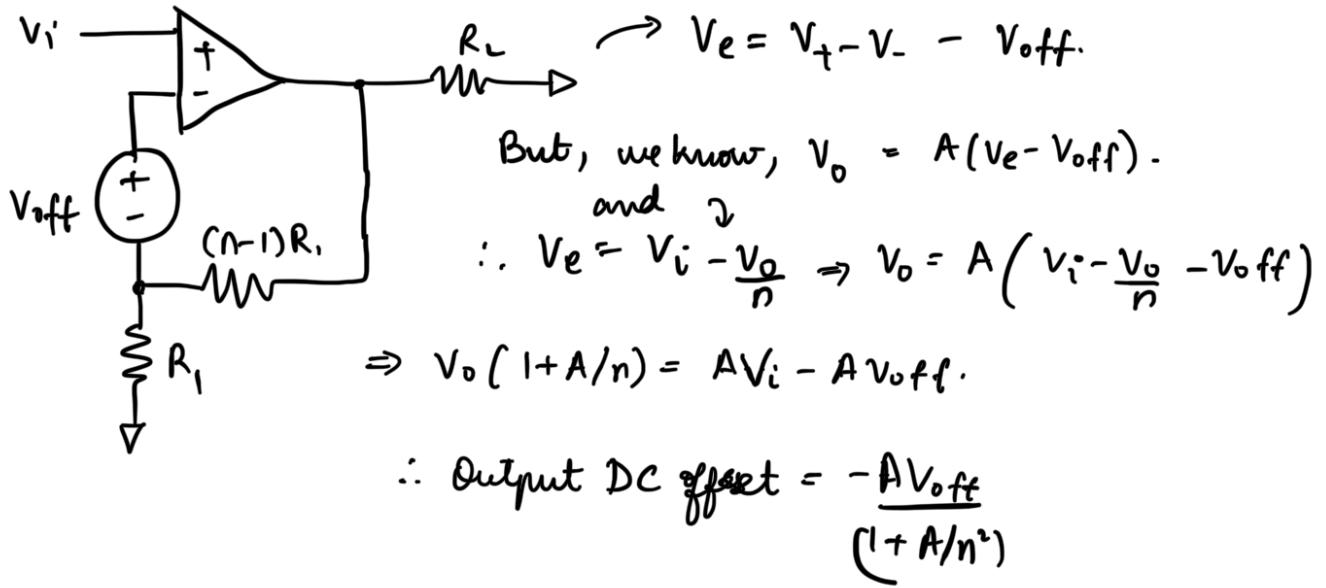


* Negative feedback (DC) [as the offset is DC] around the op amp is absolutely essential to set the opamp's operating point in the high gain region.


↓
Since the offset is DC, The operating point is also called the DC point.

Integrator using an op-amp.

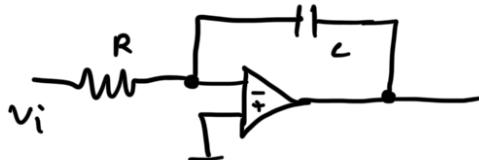Usually a Capacitor or an inductor, but see:




$$V_o = -\frac{1}{sCR} \cdot V_i$$

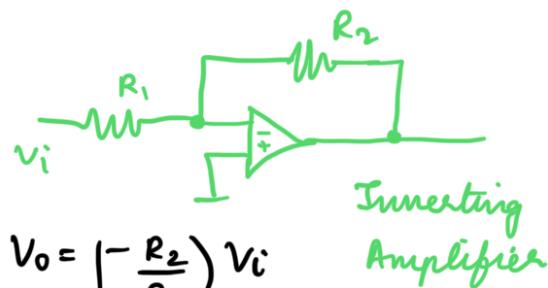

$$V_o = -\frac{R_2}{R_1} V_i$$

$$V_o(t) = -\frac{1}{CR} \int V_i dt$$

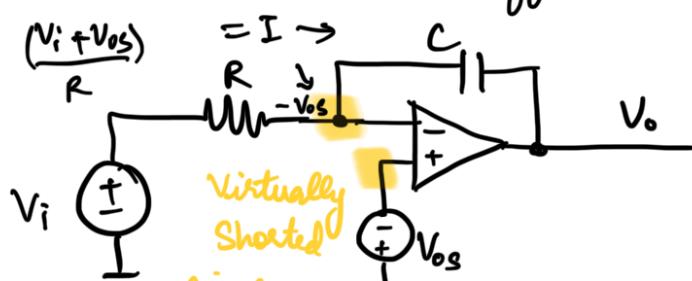Another thing : Integrator has no DC feedback !! and the OpAmp's offset also.



$$V_o = \frac{1}{C} \int \left(\frac{V_i + V_{\text{offset}}}{R} \right) dt$$

Since
OpAmp is in
-ve feedback


Problem: Even with $V_i = 0$, $V_c = \frac{1}{C} \int \frac{V_{os}}{R}$, And $V_o = -V_{os} - \frac{1}{C} \int \frac{V_{os}}{R} dt$

So the circuit will not work. [If this is the only circuit that's there]. How how how ???

In one of the labs, we will use this circuit, along with another "non-linear" circuit, that won't let it go to saturation. So, without something else giving feedback, this circuit will not work.

The integrator alone doesn't work. But however, it can work for some time, when it is in the region in between the saturation levels (V_{DD} & V_{SS})

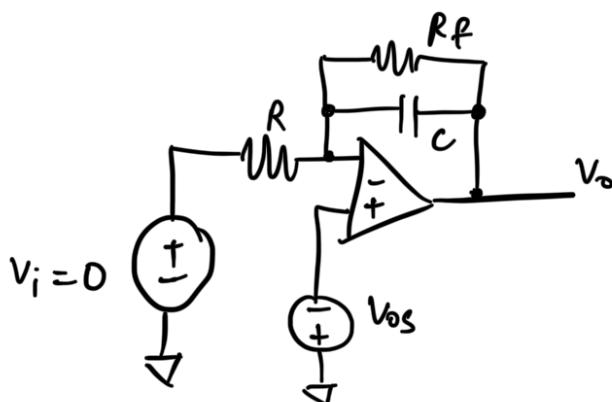Now, let's think of a way to give negative feedback to one Integrator's OpAmp [DC negative feedback] -



Maybe, add a resistor?
Hm m, let's try.

But now, is this an integrator?? Ouch.
let's see if that's true.

$$\frac{V_o}{V_i} = -\frac{1}{R(sC + 1/R_f)} = \frac{-R_f/R}{1 + sCR_f} \sim [\text{Low pass filter}]$$

Transfer function of

a) Ideal Integrator $\frac{V_o}{V_i} = \frac{-1}{sCR}$


Let's Bode Plot!




b) Real integrator

$$\frac{V_o}{V_i} = \frac{R_f/R}{1 + sCR_f}$$

Real \approx Ideal

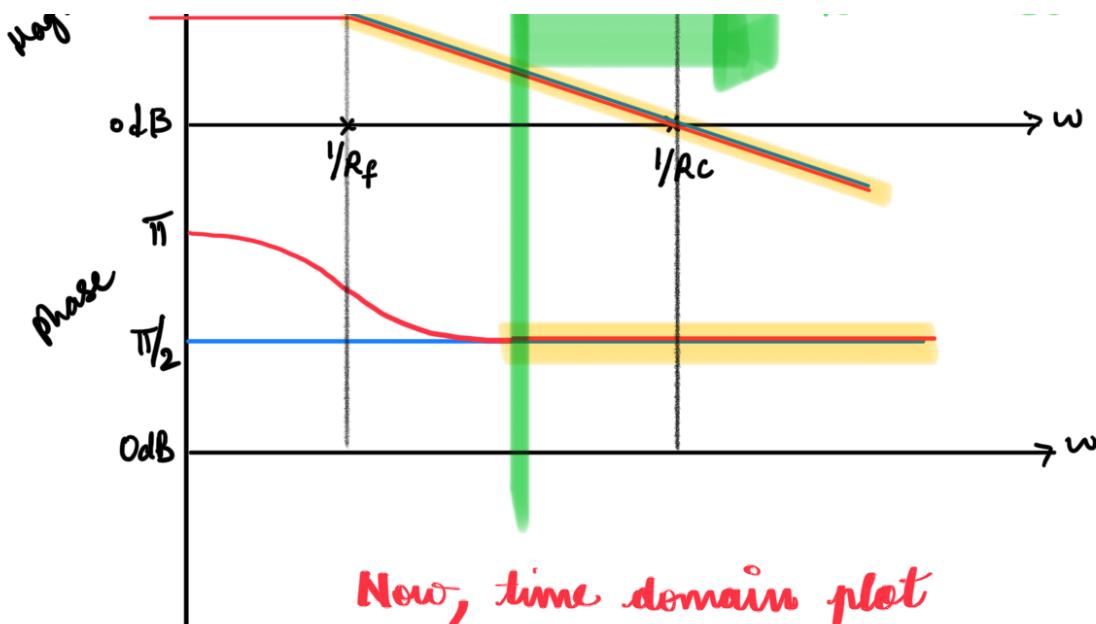

Now, time domain plot

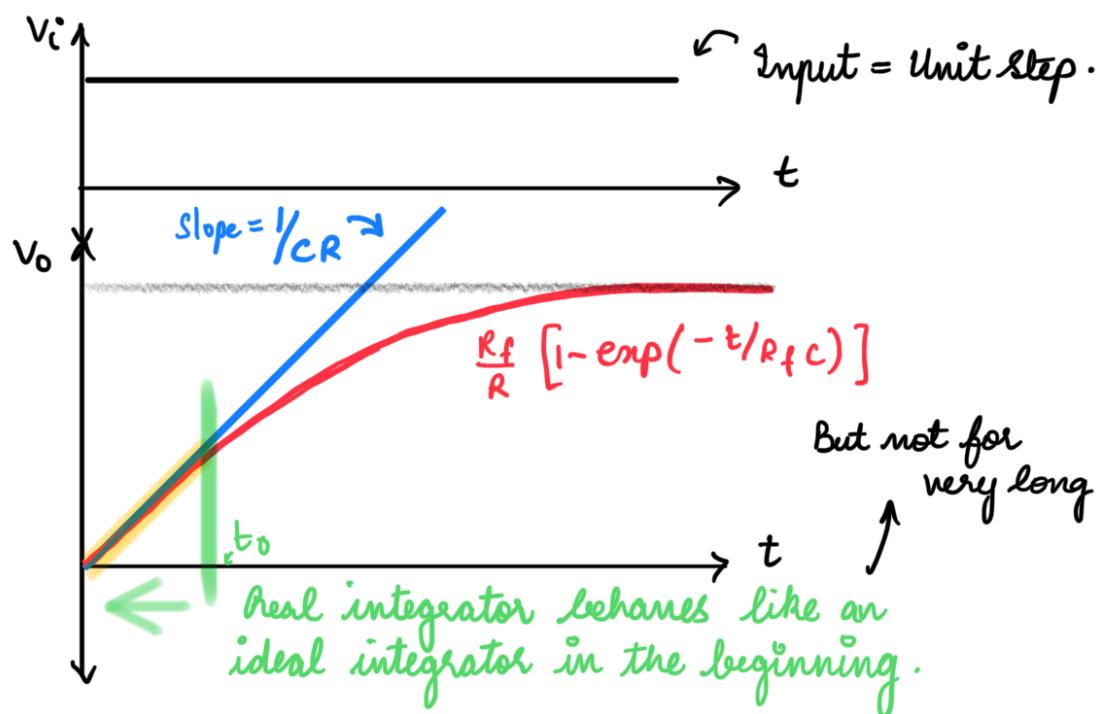


DC gain of an integrator = ∞

[Recap Pole zero graph and related stuff].

For stability, the poles must lie on the left half of s-plane.
Please take a look at this from EE1101.


Made an Oscillator in the Lab:

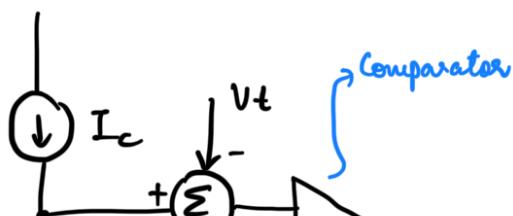


To realize a comparator, we use a saturating OpAmp.

$|V_{DD}$

V_{DD}

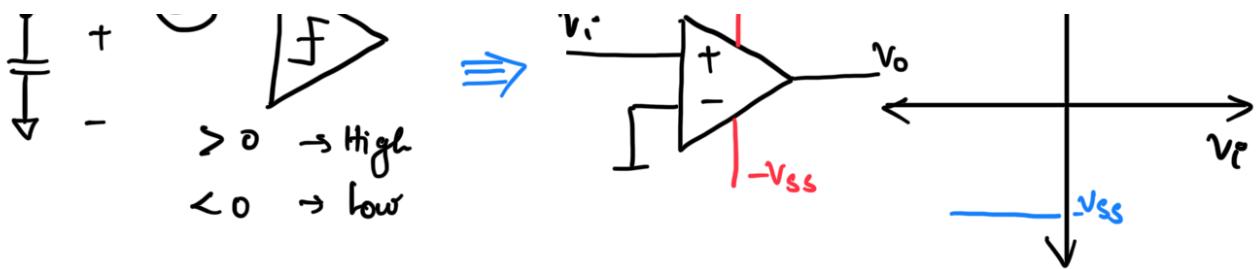

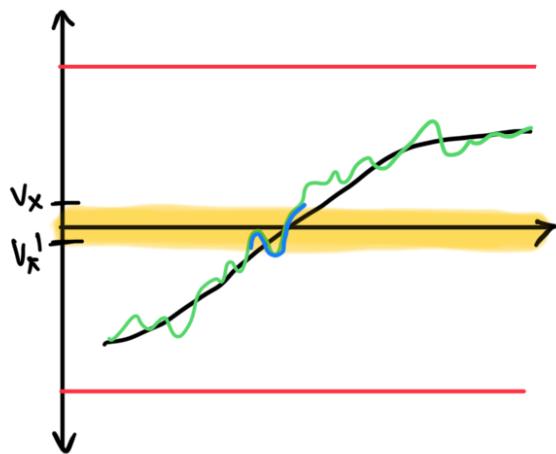Now, for the Opamp to become a Comparator:



- Ideal smooth signal
- Real, jittery signal
- The boundary of Comparison.

(Q) How to figure out "firmly" what value should we give for the blue part of the green signal?

Basically what we'll do is that, we keep the threshold [Be O/p high] as something higher than the actual threshold.

||| for lower o/p, look at a threshold, which is a bit lesser than the actual threshold.

This is what we call - Hysteresis.

When v_i is rising, look for: [if $(v_i > V_x > 0)$]


When v_i is falling, look for: [if $(v_i < V_x' < 0)$]

✓ Refer the above graph,
see y-axis.

We will realise this Hysteresis Comparator
in the next class.


In the previous note, [Analog notes 2], I understand how we get $\frac{v_o}{v_i} = \frac{1}{sCR}$ for an ideal integrator.

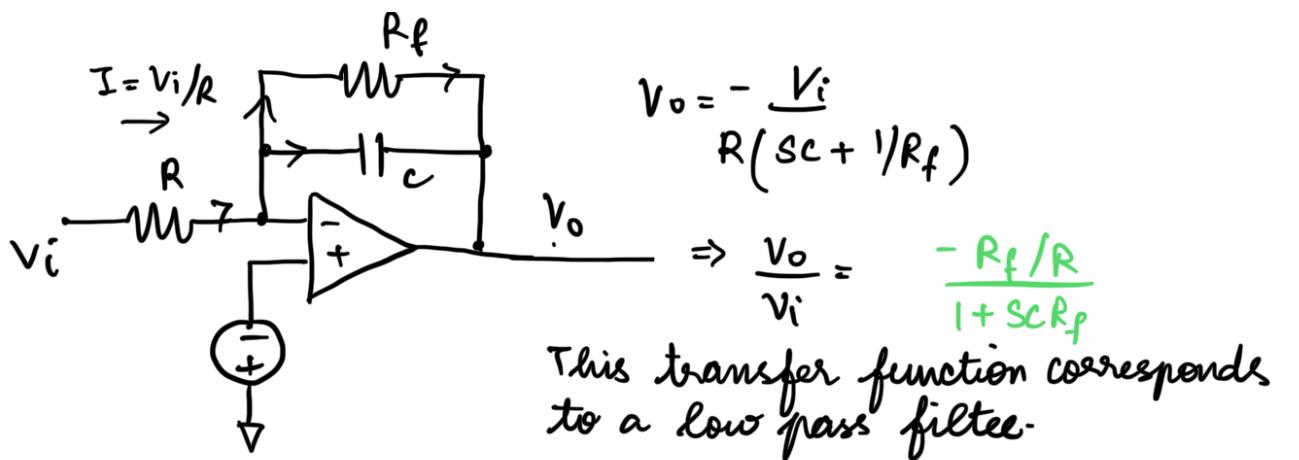But I didn't understand for real integrator. Now I understand, and I'll explain below:



When $R_f = R$, $\frac{V_o}{V_i} = -\frac{1}{1+sCR}$ → similar to the ideal case if $sCR \gg 1$.
Is this correct?

Differentiator:

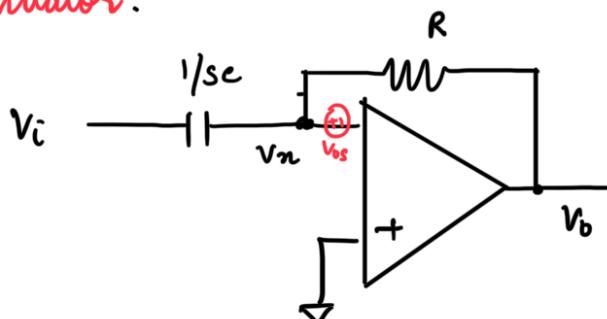

Suppressing the offset voltage - Possible.

But measuring the offset accurately and connecting it to the negative feedback terminal of the OpAmp is way more difficult - Not within the scope of this course.

Now: What is this ??

See Saurabh's Notes and write over here properly.

