

Electric Circuits & Networks

1) Voltage and Current Laws:

KVL and KCL

Tellegen's theorem : $\sum P_{\text{absorbed}} = \sum P_{\text{supplied}} \Rightarrow \sum P = 0$

Impedances in series and Admittances in parallel = Algebraic Sum.

Resistances & Inductances - Impedances, Capacitances - Admittances.

2) Basic Nodal and Mesh Analysis:

Nodal analysis:

$$\text{At node 1: } \frac{V_1 - 10}{5} + \frac{V_1}{5} + Y_{11}V_1 + \frac{V_1 - V_2}{10} + Y_{12}V_2 = 0$$

$$V_1 \left(\frac{2}{5} + \frac{1}{10} + Y_{11} \right) + \left(-\frac{1}{10} + Y_{12} \right) V_2 = 2$$

$$\Rightarrow V_1 (0.4 + 0.1 + 0.2) + (-0.1 - 0.05) V_2 = 2 \Rightarrow 0.7 V_1 - 0.15 V_2 = 2$$

$$\text{At node 2: } \frac{V_2 - V_1}{10} + Y_{22}V_2 + Y_{21}V_1 + \frac{V_2}{2} = 0$$

$$\Rightarrow V_2 \left(\frac{1}{10} + Y_{22} + \frac{1}{2} \right) = 0 \Rightarrow V_2 = \frac{6}{11.2} = 0.536V$$

$$\Rightarrow V_1 \left(-\frac{1}{10} + Y_{12} \right) + V_2 \left(\frac{1}{10} + Y_{22} + \frac{1}{2} \right) = 0 \Rightarrow V_1 = 2.86V$$

Mesh Analysis:

$$-7 + (i_1 - i_2) + 6 + 2(i_1 - i_3) = 0$$

$$1(i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0$$

$$-6 + 3(i_3 - i_2) + i_3 + 2(i_3 - i_1) = 0$$

Solve for i_1, i_2, i_3



$$\begin{aligned} 6i_2 - i_1 - 3i_3 &= 0 \\ 6i_3 - 2i_1 - 3i_2 &= 6 \\ 3i_1 - i_2 - 2i_3 &= 1 \end{aligned}$$

$$\begin{bmatrix} 3 & -1 & -2 \\ -1 & 6 & -3 \\ -2 & -3 & 6 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \\ 6 \end{bmatrix}$$

$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 9/13 & 4/13 & 5/13 \\ 4/13 & 14/39 & 11/39 \\ 5/13 & 11/39 & 17/39 \end{bmatrix} \begin{bmatrix} 1 \\ 0 \\ 6 \end{bmatrix} = \begin{bmatrix} 3 \\ 2 \\ 3 \end{bmatrix}$$

Supernode:

$$\text{Node 1: } (V_1 - V_2)/3 + (V_1 - V_3)/4 = -8 - 3 \text{ and of course, } V_3 - V_2 = 2.2$$


$$\text{Super node: } \frac{(V_2 - V_1)}{3} + \frac{(V_3 - V_1)}{4} + \frac{V_3}{5} + \frac{V_2}{1} = 3 + 2.5$$

Basically, in supernode + mesh, we reduce the no of nodes/ meshes.

Super mesh:

$$\text{super mesh eqn: } i_1 - i_3 = 7$$
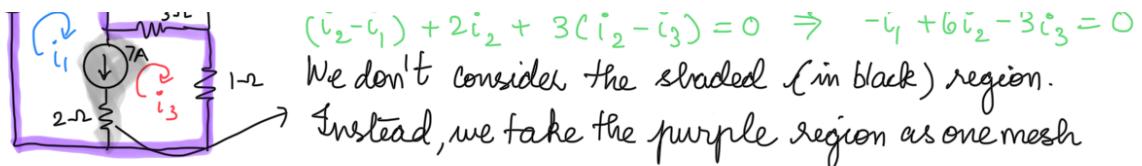
$$-7 + i_1 + 3(i_3 - i_2) + i_3 = 0 \Rightarrow i_1 - 3i_2 + 4i_3 = 7$$




3. Handy Circuit Analysis Techniques:

Linearity: A circuit that has only linear Elements (Elements whose Current/voltage depends on only 1^{st} power of current/voltage variables or the like).

Superposition: Consequence of Linearity. The response in a linear circuit having more than one independent source can be obtained by adding the responses caused by the separate independent sources acting alone.

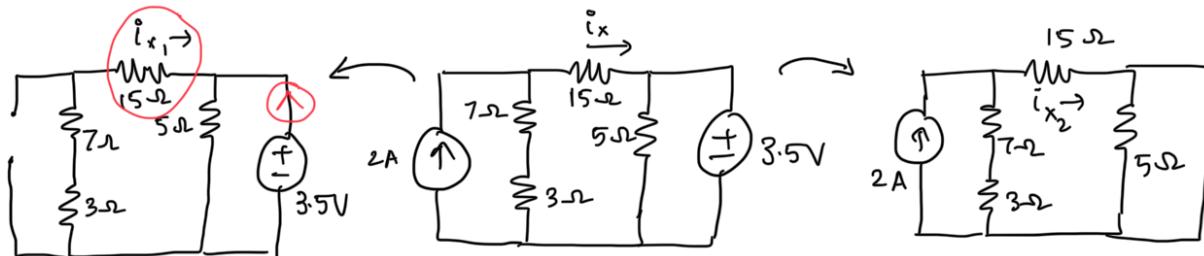Current source - Open circuited; Voltage source - close circuited -



$$R = \frac{1}{5} + \frac{1}{25} = \frac{6}{25}$$

$$R = 25/6 \Omega$$

$$\therefore I = \frac{-3.5}{25} \times 6 = \frac{-3 \times 7}{25} = \frac{-21}{25} \text{ A}$$

$$\frac{21}{25} \leftarrow \frac{5}{25} \Rightarrow i_{x_1} = -21/(25 \times 6) \text{ A}$$

$$2A \begin{cases} 15 \\ 3/5 \\ 10 \\ 2/5 \end{cases}$$


$$\Rightarrow i_{x_2} = \frac{2}{5} \times 2 = \frac{4}{5} \text{ A}$$

$$\begin{aligned} i_x &= i_{x_1} + i_{x_2} = -\frac{21/30}{5} + \frac{4}{5} = \frac{99/30}{5} \\ &= \frac{33}{50} = 0.66 \text{ A} \end{aligned}$$

The contribution of the 3.5V source does not depend on the contribution of the 2A source - Provided all of the elements used are linear.

Source Transformation

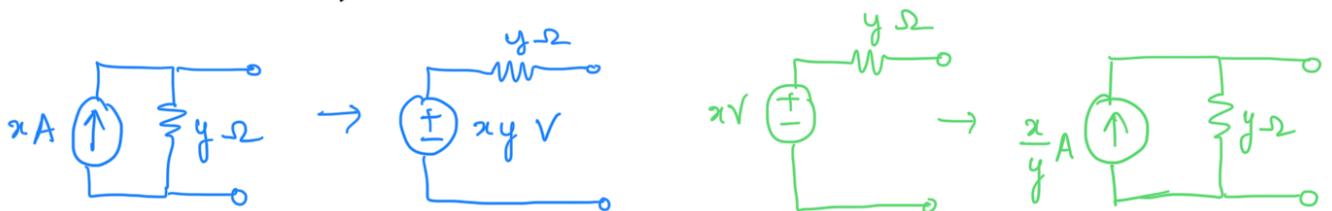A practical voltage source can be electrically equivalent to a practical current source, and vice versa.



Head of the current source \Leftrightarrow + Terminal of Voltage source

Thevenin and Norton Equivalent Circuits

Thevenin:

Replace everything except load resistor with an equivalent composed of an independent voltage source in series with a resistor




Norton:

Replace everything except load resistor with an equivalent composed of an independent current source in parallel with a resistor.



Can go from Thevenin to Norton and vice versa by source Transformations

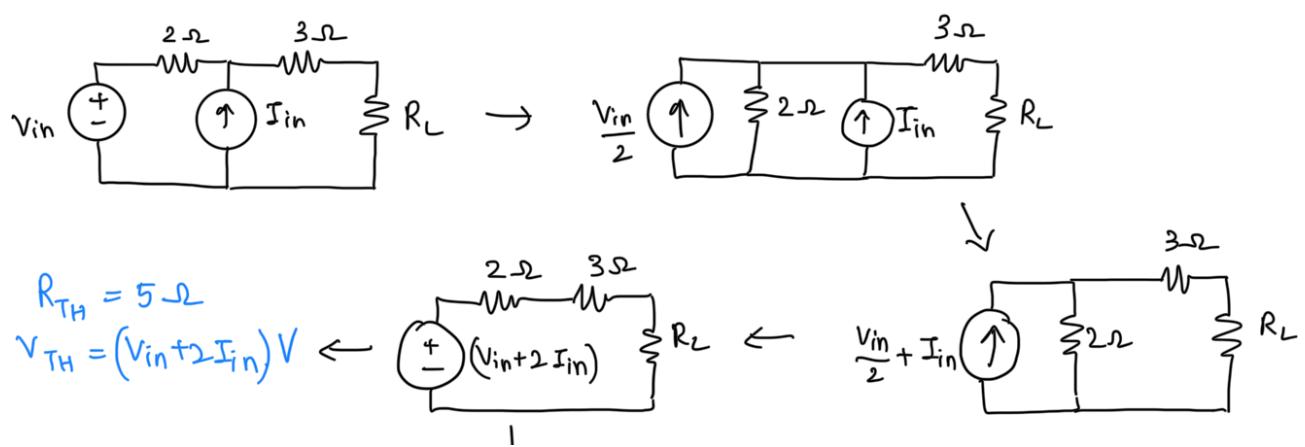How to get Thevenin and Norton Equivalents? \Rightarrow Repeated Source Transformation



$$R_N = 5\Omega$$

$$V_N = \frac{V_{in} + 2I_{in}}{5}$$



$V_{oc} = V_{open\ circuit}$, $I_{sc} = I_{short\ circuit}$

Driving point Impedance : Z_{TH} .

To find this, [According to Thévenin's Theorem] Zero out all independent sources and connect the part of the network to a source V_{oc} about which we have to find the equivalent circuit. Source is I_{sc} if Norton theorem is used.

$$V_{oc} = R_{TH} i_{sc}$$

When dependent sources are present :


Treat them like other components. Write KVL and KCL. Simplify.

At the end, we must get only an Impedance if we don't have indep. sources, but only dependent sources.

e.g.

$$-4 + 2 \times 10^3 \left(-\frac{V_x}{4000} \right) + 3k(0) + V_x = 0$$

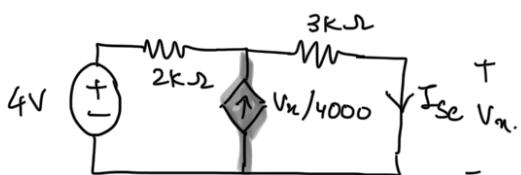
$$\Rightarrow \frac{V_x}{2} = 4 \Rightarrow V_x = 8V.$$




Since terminals are short circuited, $V_x = 0$
 \therefore Dependent source = 0
 $\therefore I_{sc} = 4 / 5 \times 10^3 = 0.8 \times 10^{-3} A.$

To get R_{TH} , we know, $R_{TH} = V_{oc} / I_{sc} = 8 / 0.8 \times 10^{-3} = 10k\Omega$


\therefore Thévenin Equivalent =

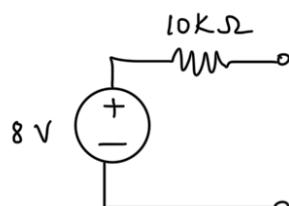

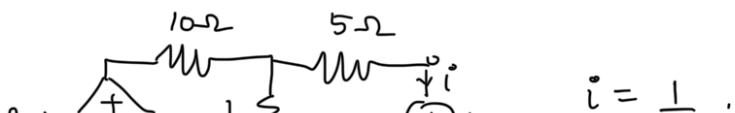Pro tip: Sometimes it might help to connect 1A [$\alpha 1V$] source across the terminals and have V_{oc} [αI_{sc}] as $1 \times R_{TH}$ [$\alpha 1/R_{TH}$], solve for V_{oc} [αI_{sc}] and then get R_{TH} .



A Quick Example!

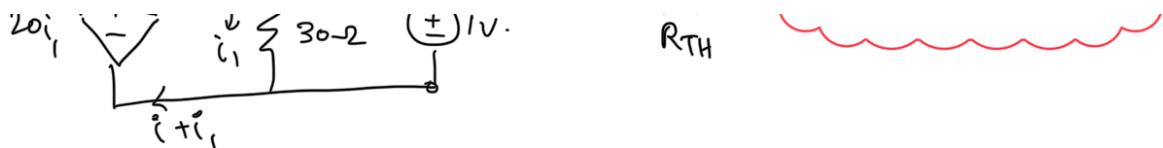

$$-20i_1 + 10(i+i_1) + 30i_1 = 0 \Rightarrow 20i_1 + 10i = 0 \Rightarrow 2i_1 = -i \quad (i_1 = -\frac{1}{2}i)$$

$$-30i_1 + 5i + 1 = 0 \Rightarrow -30(-\frac{1}{2}i) + 5i + 1 = 0 \\ \Rightarrow 20i + 1 = 0 \\ \underline{i = -1/20 \text{ A.}}$$

$$\therefore R_{TH} = 20 \Omega \quad \rightarrow$$







Maximum Power Transfer

A network delivers maximum power to a load resistance when it is equal to the Thévenin equivalent resistance of a network.

There is a distinct difference between "drawing" maximum power from a "source" and "delivering" maximum power to a "load".

(Drawing max power from a (voltage source) = Shorting the terminals)

Delta-Wye Conversion

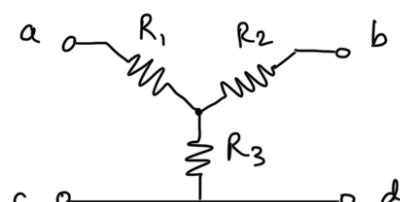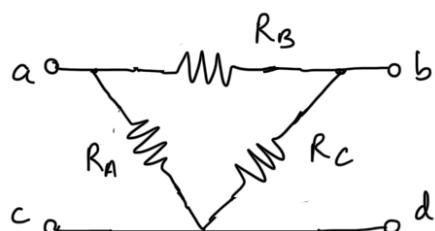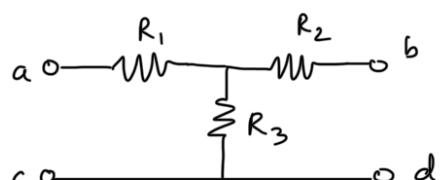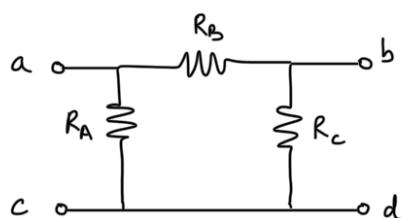

$$K_A = (K_1 K_2 + K_2 K_3 + K_3 K_1) / R_2$$

$$R_1 = R_A R_B / (R_A + R_B + R_C)$$

$$R_B = (R_1 R_2 + R_2 R_3 + R_3 R_1) / R_3$$

$$R_2 = R_B R_C / (R_A + R_B + R_C)$$

$$R_C = (R_1 R_2 + R_2 R_3 + R_3 R_1) / R_1$$

$$R_3 = R_A R_C / (R_A + R_B + R_C)$$

4) Laplace Domain

$$F(s) = \int_{-\infty}^{\infty} e^{-st} f(t) dt, \quad f(t) = \frac{1}{2\pi j} \int_{\sigma_0 - j\infty}^{\sigma_0 + j\infty} e^{st} F(s) ds$$

Initial value theorem: $\lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} [s F(s)]$

Final value theorem: $\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} [s F(s)]$.

Every analysis, except specified here, is carried out in the same manner in the laplace domain, as in time domain.

Capacitor: $i(t) = C \frac{dv}{dt} \longrightarrow I_C(s) = CS V_C(s) - C v_c(0^-)$
 $V_C(s) = \frac{I_C(s)}{SC} + \frac{v_c(0^-)}{S}$.

Impedance = $1/SC$

Inductor: $v(t) = L \frac{di}{dt} \longrightarrow V_L(s) = LS I_L(s) - L i_L(0^-)$
 $I_L(s) = \frac{V_L(s)}{SL} + \frac{i_L(0^-)}{S}$

Impedance = sL

Analysis would be done just like time domain, but inductances and capacitances would be written in Laplace domain like mentioned above, and all other elements would also undergo Laplace transform.
 $[v(t) = u(t), V(s) = 1/S]$

Poles, zeroes, transfer functions: $Z(s) = \frac{N(s)}{D(s)}$

$H(s) = \text{transfer function} = \frac{V_{out}}{V_{in}}$, Poles $\Rightarrow D(s) = 0$; Zeros $\Rightarrow N(s) = 0$.

4) Bode Plots

Quick method of obtaining an approximate picture of the amplitude and phase variation of a given transfer function as functions of ω .

We will use logarithmic scales for frequency and magnitude, providing an improved snapshot of frequency over a wide range of values.

This approximate response curve : A asymptotic / Bode plot.

The Decibel Scale

We will be using logarithmic scales for frequency and magnitude for improved snapshot of frequency response over a wide range of values.

$$|H(j\omega)| = 10^{H_{dB}/20}; \quad H_{dB} = 20 \log |H(j\omega)|$$

An increase of $|H(j\omega)|$ by a factor of 10 corresponds to an increase in H_{dB} by 20 dB.
 $H(j\omega) \leftrightarrow H(s)$ as well.

$$|H(j\omega)| = 1 \Leftrightarrow H_{dB} = 0$$

$$|H(j\omega)| = 2 \Leftrightarrow H_{dB} = 6 \text{ dB}$$

$$|H(j\omega)| = 10 \Leftrightarrow H_{dB} = 20 \text{ dB}$$

Decade : Range of frequencies defined by a factor of 10 [3 → 30]

Octave : Range of frequencies defined by a factor of 2 [7 → 14].

Determination of Asymptotes

$$H(s) = 1 + \frac{s}{a} \quad (\text{pole at } s = -a).$$

$$|H(j\omega)| = \left| 1 + \frac{j\omega}{a} \right| = \sqrt{1 + \frac{\omega^2}{a^2}} \Rightarrow H_{dB} = 20 \log \sqrt{1 + \frac{\omega^2}{a^2}}.$$


for $\omega \ll a$,

for $\omega \gg a$.

$$\underline{H_{dB} = 20 \log (1) = 0}$$

$$\underline{\frac{H_{dB}}{1} = 20 \log \left(\frac{\omega^2}{a^2} \right)^{1/2} = 20 \log \frac{\omega}{a}}$$

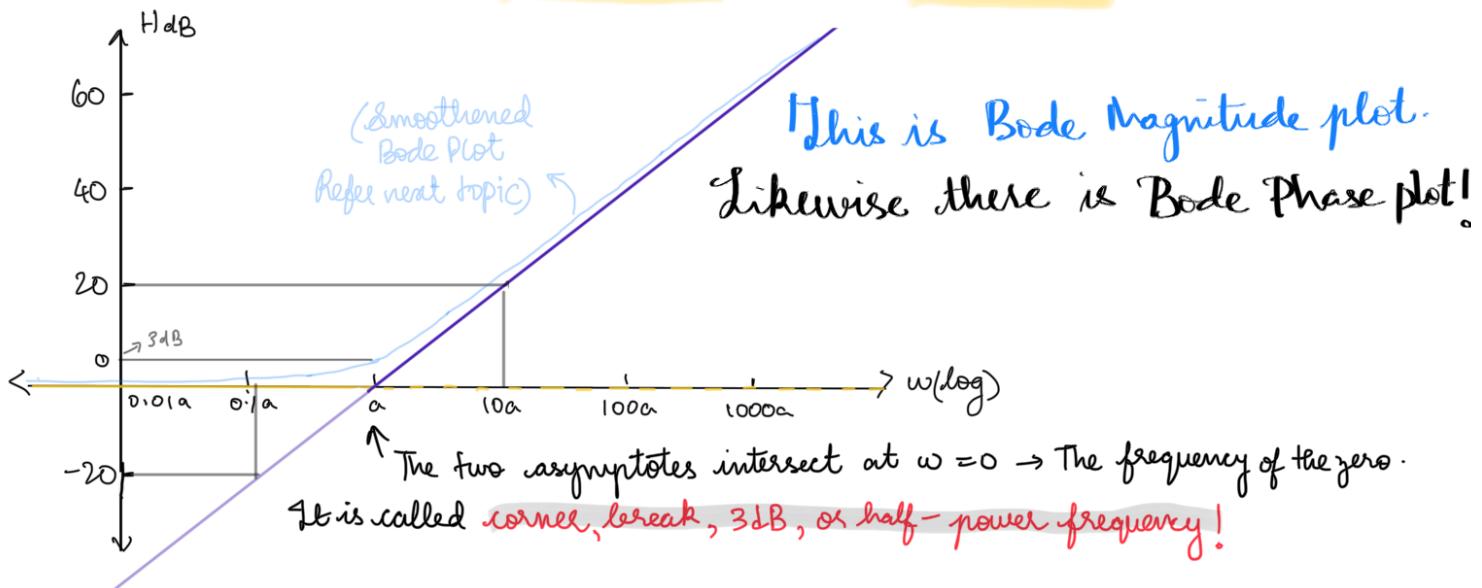or, for $\omega = a$, $H_{dB} = 0$, \leftarrow For $\omega = a$, $H_{dB} = 0$; $\omega = 10a$, $H_{dB} = 20 \text{ dB}$.
 $\omega = 2a$, $H_{dB} = 6 \text{ dB}, \dots \rightarrow 6 \text{ dB/octave!}$ $\rightarrow 20 \text{ dB/decade}$ Both are same!



Smoothing Bode Plots

We have seen for $\omega \gg a$ and $\omega \ll a$ only \Rightarrow approximations. Now, for $\omega = a$,


$$H_{dB} = 20 \log \sqrt{1 + \frac{\omega^2}{a^2}} = 20 \log \sqrt{2} = \frac{1}{2} 20 \log 2 = \frac{1}{2} \times 6 \text{ dB} = 3 \text{ dB}.$$

Now, for $\omega = 0.5a$, $H_{dB} = 20 \log \sqrt{1.25} \approx 1 \text{ dB}$. $|H(j\omega)| = \sqrt{2}$, $H_{dB} = 3 \text{ dB}$

Phase Response

$$\text{ang } H(j\omega) = \text{ang} \left(1 + j\frac{\omega}{a} \right) = \tan^{-1} \frac{\omega}{a}$$

For $\omega \ll a$, $\text{ang } H(j\omega) = 0^\circ \rightarrow$ for $\omega < 0.1a$ || For $\omega \in [0.1a, 10a]$, Slope = $45^\circ/\text{decade}$.
 For $\omega \gg a$, $\text{ang } H(j\omega) = 90^\circ \rightarrow$ for $\omega > 10a$ || [as $\omega = a \Rightarrow \text{ang } H(j\omega) = 45^\circ$]

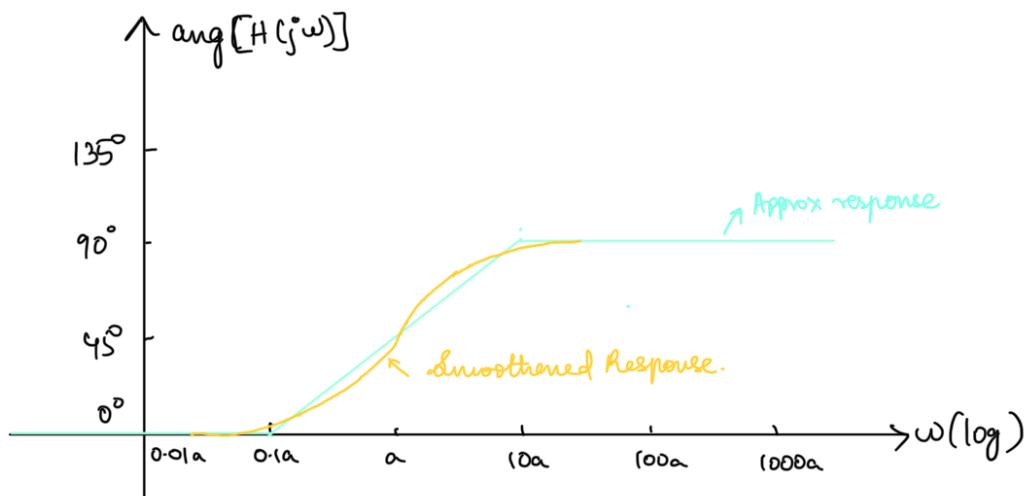

Bode plots with multiple terms

For transfer functions with more than a simple pole \rightarrow Bode method


$$H(s) = K \left(1 + \frac{s}{s_1}\right) \left(1 + \frac{s}{s_2}\right) \Leftrightarrow H_{dB} = 20 \log K + 20 \log \sqrt{1 + \left(\frac{\omega}{s_1}\right)^2} + 20 \log \sqrt{1 + \left(\frac{\omega}{s_2}\right)^2}$$

Plot everything and add all the asymptotes. Refer to this for each pole:

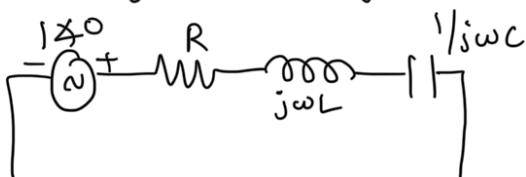6) Resonance (Parallel and series)

Frequency Response of Circuits:

$$Z(j\omega) = R + j(\omega L - 1/\omega C)$$




$$I = \frac{1}{R + j(\omega L - 1/\omega C)}$$

$$|I| = \frac{1}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

$$= \frac{e^{-j \arg Z(j\omega)}}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

For $\omega L = \frac{1}{\omega C}$, or $\omega_0 = 1/\sqrt{LC}$, $|I| = 1/R$ Purely Resistive.

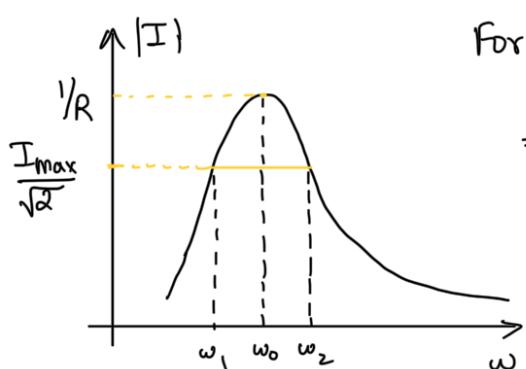

For $|I| = I_{max}/\sqrt{2} \Rightarrow 1/\sqrt{2}R = |I|$.

$$\Rightarrow R^2 + (\omega L - 1/\omega C)^2 = 2R^2$$

$$(\omega L - 1/\omega C)^2 = R^2$$

$$\Rightarrow (\omega L - 1/\omega C) = \pm R$$

$$\Rightarrow \omega^2 LC - 1 = \omega RC, \quad \omega^2 - \frac{\omega R}{L} - \frac{1}{LC} = 0,$$

$$\omega^2 LC - 1 = -\omega RC \quad \omega^2 + \frac{\omega R}{L} - \frac{1}{LC} = 0$$

$$\Rightarrow \omega_{11} = \frac{R}{2L} + \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}} \quad ; \quad \omega_{12} = \frac{R}{2L} - \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$$

$$-\sqrt{4L - LC}$$

$$\sqrt{4L - LC}$$

$$\omega_{21} = -\frac{R}{2L} + \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}} ; \quad \omega_{22} = -\frac{R}{2L} - \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$$

$$(\alpha = R/2L ; \omega_0 = 1/\sqrt{LC}) : \quad \omega_1 = \omega_{21} = -\alpha + \sqrt{\alpha^2 + \omega_0^2}$$

$$\omega_2 = \omega_{22} = \alpha + \sqrt{\alpha^2 + \omega_0^2}$$

Bandwidth: $B = \omega_2 - \omega_1 = 2\alpha$

Quality factor: $Q = \omega_0/B = \omega_0/2\alpha = \frac{1}{R}\sqrt{\frac{L}{C}}$

7) Two port networks

Impedance parameters (Z) $V_1 V_2 I_1 I_2$

$$V_1 = Z_{11}I_1 + Z_{12}I_2 ; \quad V_2 = Z_{21}I_1 + Z_{22}I_2$$

Reciprocity: $Z_{12} = Z_{21}$, Symmetry: $Z_{11} = Z_{22}$

Series-series connection: $Z = Z_1 + Z_2$

Admittance parameters (Y) = $1/Z \quad I_1 I_2$
 $V_1 V_2$

$$I_1 = Y_{11}V_1 + Y_{12}V_2 ; \quad I_2 = Y_{21}V_1 + Y_{22}V_2$$

Reciprocity: $Y_{12} = Y_{21}$, Symmetry: $Y_{11} = Y_{22}$

Parallel-parallel connection: $Y = Y_1 + Y_2$

Hybrid Parameters (h) $V_1 I_2 \quad I_1 V_2$

$$V_1 = h_{11}I_1 + h_{12}V_2 ; \quad I_2 = h_{21}I_1 + h_{22}V_2$$

Reciprocity: $h_{12} = -h_{21}$, Symmetry: $|H| = 1$


Series-parallel connection: $H = H_1 + H_2$

Inverse hybrid Parameters (g) = $1/H \quad V_2 I_1$
 $V_1 I_2$

$$I_1 = g_{11}V_1 + g_{12}I_2 ; \quad V_2 = g_{12}V_1 + g_{22}I_2$$

Reciprocity: $g_{12} = -g_{21}$, Symmetry: $|G| = 1$

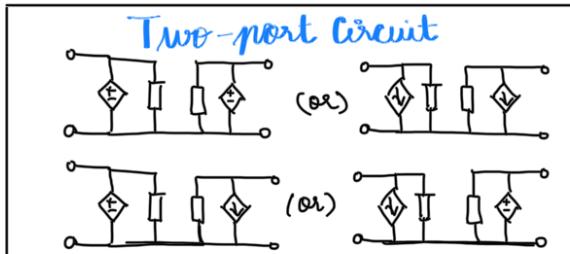Parallel-series connection: $G = G_1 + G_2$



Interconnection of Networks


Series-series: $1a' \rightarrow 2a, 1b' \rightarrow 2b$

Series-parallel: $1a' \rightarrow 2a, 1b \rightarrow 2b, 1b' \rightarrow 2b'$

Parallel-series: $1b' \rightarrow 2b, 1a \rightarrow 2a, 1a' \rightarrow 2a'$

Parallel-parallel: $1ab \rightarrow 2ab, 1ab' \rightarrow 2ab'$

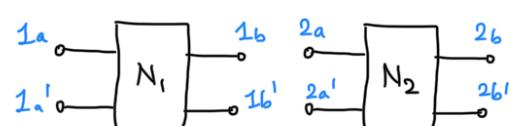Cascade: $1b \rightarrow 2a, 1b' \rightarrow 2a'$.



$$H = \frac{1}{Z_{22}} \begin{bmatrix} |Z| & Z_{12} \\ -Z_{21} & 1 \end{bmatrix}$$

$$Z = \frac{1}{h_{22}} \begin{bmatrix} |H| & h_{12} \\ -h_{21} & 1 \end{bmatrix}$$

$$G = \frac{1}{Z_{11}} \begin{bmatrix} 1 & -Z_{12} \\ Z_{21} & |Z| \end{bmatrix}$$

$$Z = \frac{1}{g_{11}} \begin{bmatrix} 1 & -g_{12} \\ g_{21} & |G| \end{bmatrix}$$

Transmission Parameters (t) $V_1 I_1 \quad V_2 I_2$

$$T = \frac{1}{Z_{21}} \begin{bmatrix} Z_{11} & |Z| \\ 1 & Z_{22} \end{bmatrix}$$

$$V_1 = t_{11} V_2 + t_{12} I_2 ; \quad I_1 = t_{21} V_2 + t_{22} I_2$$

Reciprocity: $|T|=1$, Symmetry $= t_{11} = t_{22}$
 Cascade interconnection: $T = T_1 \times T_2$.


$$Z = \frac{1}{t_{21}} \begin{bmatrix} t_{11} & |T| \\ 1 & t_{22} \end{bmatrix}$$

8) RL, RC, RLC Circuits


Natural Response - In the absence of all sources

Forced Response - describes the contribution from external sources.

Complete Response (V or I) = Natural Response + Forced Response

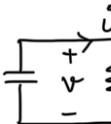RC: $C \frac{dv}{dt} + \frac{v}{R} = 0$  ; Energy = $\frac{1}{2} C V_0^2$, $\tau = RC \rightarrow e^{-t/\tau}$

$$\Rightarrow \frac{dv}{v} = -\frac{1}{RC} dt \Rightarrow v(t) = V_0 e^{-t/RC}$$

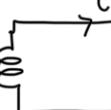RL: $L \frac{di}{dt} + R i = 0$  ; Energy = $\frac{1}{2} L I_0^2$, $\tau = L/R$.

$$\Rightarrow \frac{di}{i} = -\frac{R}{L} dt \Rightarrow i(t) = I_0 e^{-t/(L/R)}$$

If general Perspective: $\tau = \text{Req } C$ (or) $\tau = L/\text{Req}$.

(L or C)

source free RC and RL circuit with single Energy Storage Element

1. Determine Req using Thvenin equivalent, then τ .

2. Find initial conditions of $v(t)$ or $i(t)$.

3. Solution = $v(t) = v(0+) e^{-t/\tau}$ or $i(t) = i(0+) e^{-t/\tau}$.

Initial Conditions

imposed when source is unit step or $[u(t)]$

Capacitor: $i(0^-) = i(\infty) = 0$; $v(0^-) = v(0^+)$ [Resists change in V]
 open circuit $i(0^+) = C(dv/dt)$ Capacitor becomes voltage source!


Inductor: $v(0^-) = v(\infty) = 0$; $i(0^-) = i(0^+)$ [Resists change in I]
 short circuit $v(0^+) = L(di/dt)$ Inductor becomes current source!

(Resistor - Reacts Instantaneously)

Forced Response of RC

Let's assume that the forced response is some const.
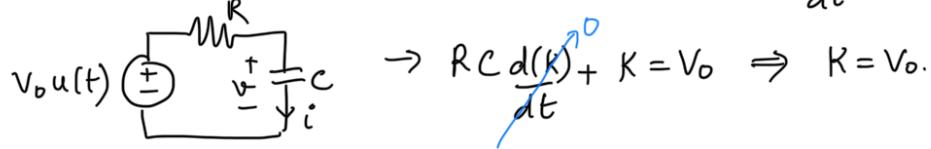
$$V_f = K \text{ (let's assume)} \Rightarrow \text{In RC, } RC \frac{dv}{dt} + v = V_0$$



Complete Response of RC

$$V_{\text{total}} = V_n + V_f; \quad V_n = A e^{-t/\tau}; \quad V_f = V_0; \quad V_{\text{total}} = A e^{-t/\tau} - V_0.$$

$\rightarrow t < 0, u(t) = 0$ no?


$$\text{Initial Conditions: } v(0^+) = 0 \Rightarrow V_{\text{total}}(0) = 0 = A + V_0 \Rightarrow \underline{A = -V_0}$$

$$\therefore V_{\text{total}}(t) = (1 - e^{-t/\tau}) V_0 \text{ and similarly for RL, } i_{\text{total}}(t) = \frac{V_0}{R} (1 - e^{-Rt/L})$$

Procedure for Complete Response (For RL and RC)

1. Find τ by finding Thvenin equivalent [Req Ceq or L_{eq}/R_{eq}]
2. Determine initial conditions [Capacitor - V, Inductor I]
3. Determine final conditions [Cap - $v(\infty)$, Ind. - $i(\infty)$]
4. Final Response = $v(t) = v(\infty) + [v(0^+) - v(\infty)] e^{-t/\tau}$
 $i(t) = i(\infty) + [i(0^+) - i(\infty)] e^{-t/\tau}$

RLC Circuits (series)

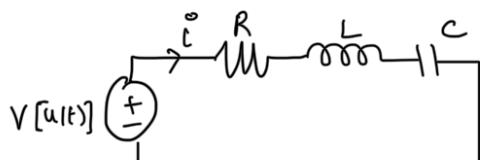

$$V = V_R + V_L + V_C; \quad i = i_C = C \frac{dV_C}{dt}.$$

$$V_R = iR = RC \frac{dV_C}{dt}, \quad V_L = L \frac{di}{dt} = L \frac{d}{dt} \left[C \frac{dV_C}{dt} \right] = LC \frac{d^2V_C}{dt^2}$$

$$\therefore V = LC \frac{d^2V_C}{dt^2} + RC \frac{dV_C}{dt} + V_C \Rightarrow \frac{V}{LC} = \frac{d^2V_C}{dt^2} + \frac{R}{L} \frac{dV_C}{dt} + \frac{V_C}{LC}.$$

Solving for V_C in the S domain for natural response, we get:

$$S^2 V_C + \underline{R} s V_C + \underline{1} V_C = 0 \Rightarrow S^2 + R s + \underline{1} = 0$$

$$S = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \quad [\alpha = R/2L, \omega_0 = 1/\sqrt{LC}]$$

$$\text{Damping Factor} = \frac{\alpha}{\omega_0} = \xi = 1/2Q$$


Case 1: $\alpha^2 > \omega_0^2$: Overdamped, $S = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$, Real, -ve roots
 $V_c(t) = A_1 e^{-s_1 t} + A_2 e^{-s_2 t}$

Case 2: $\alpha^2 = \omega_0^2$: Critically damped, $S = -\alpha$, Real, -ve & equal roots.
 $V_c(t) = (A_1 t + A_2) e^{-\alpha t}$

Case 3: $\alpha^2 < \omega_0^2$: Underdamped, $S = -\alpha \pm i\sqrt{\alpha^2 - \omega_0^2}$, Imaginary Roots are complex conjugates of each other
 $V_c(t) = [A_1(\cos \beta t + i \sin \beta t) + A_2(\sin \beta t - i \cos \beta t)] e^{-\alpha t}$
 ↗ Re part only considered in real circuits
 $\text{Re}[V_c(t)] = e^{-\alpha t} [A_1 \cos \beta t + A_2 \sin \beta t], \beta = \sqrt{\omega_0^2 - \alpha^2}$ Taking only the real parts

Case 4: $R=0 \Rightarrow S = \pm i\omega$, Purely imaginary, $V_c(t) = A_1 \cos \omega t + A_2 \sin \omega t$

RLC Circuits (Parallel)

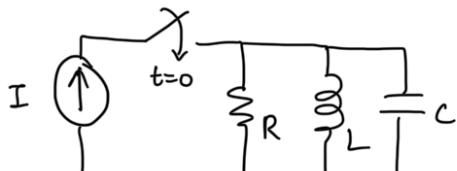

$$I = \frac{V_c}{R} + \frac{1}{L} \int V_c dt + \frac{C}{dt} \frac{dV_c}{dt}$$

(differentiate)

$$\frac{1}{R} \frac{dV_c}{dt} + \frac{1}{L} V_c + C \frac{d^2 V_c}{dt^2} = 0.$$

$$\Rightarrow \frac{d^2 V_c}{dt^2} + \frac{1}{RC} \frac{dV_c}{dt} + \frac{1}{LC} V_c = 0 \Rightarrow S^2 V_c + \frac{S}{RC} V_c + \frac{1}{LC} V_c = 0$$

$$\Rightarrow S^2 + \frac{1}{RC} S + \frac{1}{LC} = 0 \Rightarrow S = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$(\alpha = 1/2RC, \omega_0 = 1/\sqrt{LC}) \Leftarrow = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$

The same 3 cases for parallel, except Case 4

Complete Response of RLC

1. Determine the initial conditions
2. Obtain a numerical value for the forced response
3. Write the form of natural response with unknown constants A_1, A_2, \dots [Find α, ω_0, β] (which case also)
4. Forced + Natural = Total

5. Find $\dot{v}(0)$ or $v(0)$ and $\frac{d\dot{i}(0)}{dt}$ or $\frac{dv(0)}{dt}$ and put initial conditions to get A_1, A_2 , etc.

To find $\frac{dv(0)}{dt}$ or $\frac{d\dot{i}(0)}{dt}$ might be tricky. \Rightarrow If $\frac{dv(0)}{dt}$, relate with capacitor current $\frac{di(0)}{dt} \rightarrow$ inductor voltage.

9) Sinusoidal Steady State (All about Phasors)

Steady state response = Forced Response.

Steady state \neq not changing with time

Steady state = Reached after transient / natural response die out

Transient Response = Natural Response

The Phasor

$$I_m \cos(\omega t + \phi) = I_m \angle \phi$$

Phasor transformation: $I_m \cos(\omega t + \phi) \rightarrow I_m e^{j\omega t + j\phi}$
 $\text{Re}\{i(t)\} = I_m e^{j\phi} \rightarrow I_m \angle \phi$.



$$\text{Re}\{I_m e^{j(\omega t + \phi)}\} = I_m \cdot \text{Re}\{\cos(\omega t + \phi) + j \sin(\omega t + \phi)\} = I_m \cos(\omega t + \phi).$$

$$\text{Resistor: } \bar{V} = R \bar{I}, \text{ Inductor: } \bar{V} = j\omega L \bar{I}, \text{ Capacitor: } \bar{V} = \frac{\bar{I}}{j\omega C} = -j \frac{I}{\omega C}$$

Impedance = Resistance + j Reactance

Admittance = Conductance + j Susceptance

Phasor Diagrams

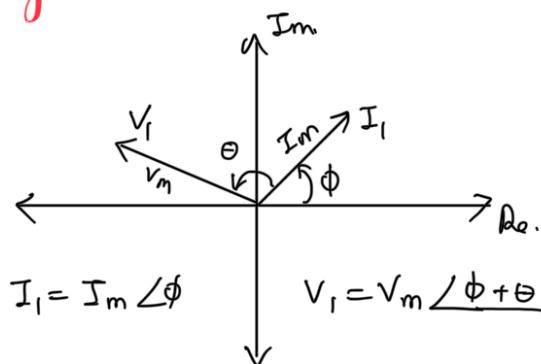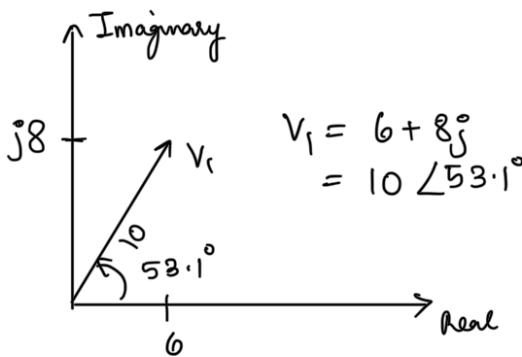

10) Power Analysis

Instantaneous Power = $p(t) = v(t)i(t)$.

$$\text{Average power } P = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} p(t) dt = \frac{1}{2} V_m I_m \cos(\theta - \phi)$$

$$P = \frac{1}{2} \operatorname{Re} \{ VI^* \}$$

Average power absorbed by purely reactive elements = 0.

Maximum Power Transfer: ($Z_{TH} = R_{TH} + j X_{TH}$)

An independent voltage source in series with Z_{TH} or an independent current source in parallel with Z_{TH} , delivers a maximum average power to a load Z_L , when $Z_L = Z_{TH}^*$

Impedance matching is done to make $Z_L = Z_{TH}^*$ for maximum power transfer by adding **parallel capacitor** and **series inductor**, which will be added to Z_{TH} and Z_L to make them complex conjugates!

Effective Values of I and V (rms)

$$I_{eff} = I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}, \quad V_{eff} = V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2 dt}$$

$$= I_m / \sqrt{2} \quad \quad \quad = V_m / \sqrt{2}$$

$$\Rightarrow P = \frac{1}{2} V_m I_m = V_{eff} I_{eff}$$

$$= V_{eff}^2 / R = I_{eff}^2 R.$$

Apparent power and power Factor (X)

Apparent power = $V_{eff} I_{eff}$; Average Power = $V_{eff} I_{eff} \cos \phi$.

$$\therefore PF = \cos \phi = P / I_{eff} V_{eff}$$

Lagging PF = inductive. Leading PF = capacitive.

$$\text{Complex power} \quad \bar{S} = \bar{V}_{eff} \bar{I}_{eff}^* \Rightarrow \bar{S} = V_{eff} I_{eff} \angle \phi$$

$$\bar{S} = P + jQ, \quad P = \text{Average power}, \quad Q = \text{Reactive power}.$$

$$P = V_{\text{eff}} I_{\text{eff}} \cos \phi, \quad Q = V_{\text{eff}} I_{\text{eff}} \sin \phi.$$

Sign of $Q \Rightarrow Q = -\text{ve}, \text{ capacitive load}, \quad Q = +\text{ve}, \text{ inductive load}.$

Summary of diff. powers

Quantity	Symbol	formula	Units
Average power	P	$V_{\text{eff}} I_{\text{eff}} \cos \phi$	Watt (W)
Reactive power	Q	$V_{\text{eff}} I_{\text{eff}} \sin \phi$	volt-amp-reactive (VAR)
Complex power	\bar{S}	$P + jQ$ $V_{\text{eff}} I_{\text{eff}} \angle \phi$ $\bar{V}_{\text{eff}} \bar{I}_{\text{eff}}^*$	volt-amp.
Apparent power	$ S $	$V_{\text{eff}} I_{\text{eff}}$	volt-amp.
$\bar{S} = \bar{S}_1 + \bar{S}_2 = V I_1^* + V I_2^* = (V_1 + V_2) I^*$ (parallel) (series)			

Power factor compensation

To make PF close to 1 (making it close to 1 means fully resistive), we do this compensation where we add $S_2 = jQ_2$ to $S_1 = P + jQ_1$, such that $(Q_1 + Q_2)$ is less.

If $Q_1 = +\text{ve}$, $Q_2 = \text{leading PF (capacitor) in Parallel}$
 If $Q_1 = -\text{ve}$, $Q_2 = \text{lagging PF (inductor) in Series.}$

II) Polyphase Circuits :

ab = line, AB = phase
(an)

Y Connection : $V_{an} = V_p \angle 0^\circ$ [Phase Voltage],
 $(V\sqrt{3} + 30^\circ)$ $V_{AB} = \sqrt{3} V_{an} \angle 30^\circ$ [line voltage]
 Phase current = line current = $V_{an} / Z_Y = \frac{1}{\sqrt{3}} \frac{V_p \angle \phi - 30^\circ}{Z_Y}$.

Δ Connection : $V_{AB} = V_{ab} = \sqrt{3} V_{an} \angle +30^\circ$ [Phase volt = line volt]
 $(I \sqrt{3} - 30^\circ)$ $I_{AB} = V_{AB}/Z_\Delta$ (Phase current)
 $I_a = \sqrt{3} I_{AB} \angle -30^\circ$ (line current)


$Z_y = Z_\Delta / 3$

\nearrow Total Power.

$P = 3 V_p I_p$, $P_p = \text{Power per phase} = P/3$
 $= \sqrt{3} V_L I_L \times \text{PF}$. [V_L and I_L = mag. of line current & voltage].
These Formulae are for both Δ & Y

12) Magnetically Coupled Circuits

Dot Convention :

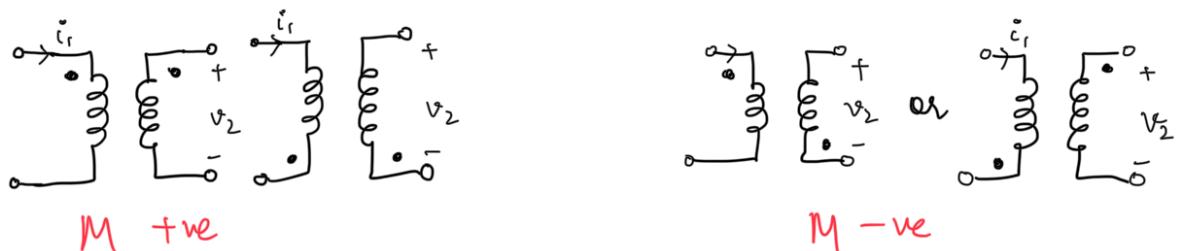

An upper limit for M and Coupling coefficient k .


$$M \leq \sqrt{L_1 L_2} \Rightarrow k = \frac{M}{\sqrt{L_1 L_2}} ; k \in [0, 1].$$

loosely coupled.

Tightly coupled


Linear Transformer: No magnetic material is involved.

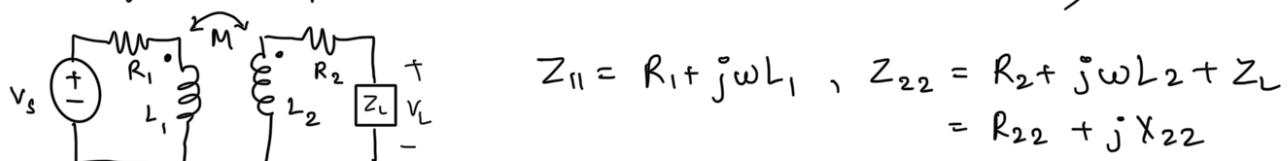
Reflected Impedance : $(R_{22} = R_2 + R_L, X_{22} = \omega L_2 + X_L)$



$$Z_{in} = Z_{11} + \frac{\omega^2 M^2}{Z_{22}} = Z_{11} + \frac{\omega^2 M^2 R_{22}}{R_{22}^2 + X_{22}^2} - j \frac{\omega^2 M^2 X_{22}}{R_{22}^2 + X_{22}^2}$$

T and Π Equivalent Circuits

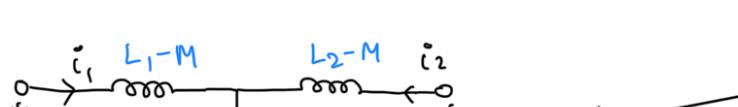


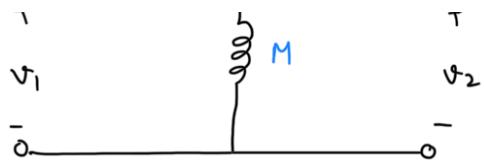

$$L_A = L_1 L_2 - M^2 / L_2 - M$$

$$L_B = L_1 L_2 - M^2 / M$$

$$L_C = L_1 L_2 - M^2 / L_1 - M$$

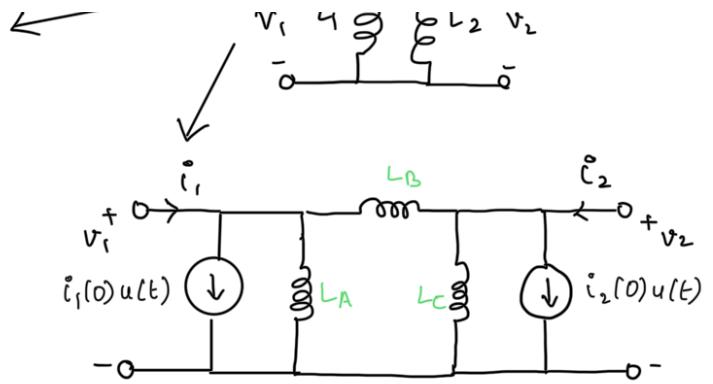

for $\vec{E}_2 \rightarrow \frac{\vec{I}_2}{\vec{I}_1} = -\frac{N_1}{N_2}$


for $\vec{E}_1 \rightarrow$

$$a = \frac{N_2}{N_1} = \frac{\bar{V}_2}{\bar{V}_1} = \frac{\bar{I}_1}{\bar{I}_2} \quad (\bar{V} = \text{Phasor})$$

Ideal Transformer:
(Turns Ratio)

$a > 1$: step-up Transformer

$a < 1$: step-down Transformer.

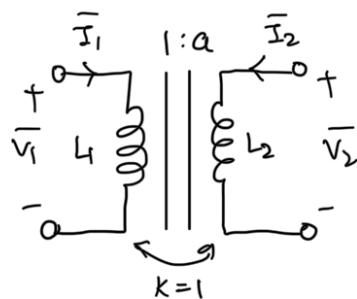

$$Z_{in} = Z_L/a^2$$

$$\bar{V}_2 \bar{I}_2 = \bar{V}_1 \bar{I}_1 \rightarrow |\bar{V}_2 \bar{I}_2| = |\bar{V}_1 \bar{I}_1| = \text{max allowable value on power transformers}$$

In time domain: $\frac{v_2}{v_1} = a \rightarrow \dot{i}_1 = -\dot{i}_2$

(II)

Equivalent Circuits

